

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -2 EXAMINATION- 2023

B.Tech-III Semester (ECE)

COURSE CODE (CREDITS): 18B11EC312(4)

MAX. MARKS: 35

COURSE NAME: Digital Electronics and Logic design

COURSE INSTRUCTORS: Munish Sood

MAX. TIME: 2 Hours

*Note: (a) All questions are compulsory.*

*(b) Marks are indicated against each question in square brackets.*

*(c) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems*

**Q1)** Design a 3 bit binary GRAY code synchronous counter using state diagram, state table and J-K flip flops. **CO-3[7]**

**Q2)** Design a 4 bit asynchronous binary Decade counter with each flip flop negatively edge triggered. Develop a timing diagram showing the Q output of each flip flop. **CO-6[5]**

**Q3)** Design a 4 bit bidirectional shift register using D flip flop. Develop a timing diagram showing the Q output of each flip flop. **CO-4[5]**

**Q4)** Design a 4 bit Digital to Analog Converter (DAC) using binary weighted resistor. A certain binary-weighted-input DAC has a binary input of 1101. If a HIGH = +3.0 V and a LOW = 0 V, what is  $V_{out}$ ? **CO-5[5]**

**Q5)** Implement the following logic expression using only NOR or NAND gates **CO-1[5]**

a)  $X = (A + B)(\bar{C} + D)(E + F)$

b)  $(AB + \bar{C})D + EF$

**Q6)** Using Boolean Algebra and De-Morgan's theorem simplify the following expressions

a)  $AB + A(B + C) + B(B + C)$

**CO-2[3]**

b)  $\overline{ABC + DEF}$

**Q7)** Use a Karnaugh map to minimize the following standard SOP 5 variable expression:

$$X = \bar{A}\bar{B}\bar{C}\bar{D}\bar{E} + \bar{A}\bar{B}\bar{C}\bar{D}E + \bar{A}\bar{B}\bar{C}D\bar{E} + \bar{A}\bar{B}\bar{C}DE + \bar{A}\bar{B}C\bar{D}\bar{E} + \bar{A}\bar{B}C\bar{D}E + \bar{A}\bar{B}CDE + \bar{A}B\bar{C}\bar{D}\bar{E} + \bar{A}B\bar{C}\bar{D}E + \bar{A}B\bar{C}D\bar{E} + \bar{A}B\bar{C}DE + \bar{A}BC\bar{D}\bar{E} + \bar{A}BC\bar{D}E + \bar{A}BCD\bar{E} + \bar{A}BCDE + ABC\bar{D}\bar{E} + ABC\bar{D}E + ABCD\bar{E} + ABCDE$$

**CO-2[5]**