

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -1 EXAMINATION- 2025

B.Tech-II Semester (CSE/IT/ECE/CE/BT/BI)

COURSE CODE (CREDITS): 18B11EC211(4)

MAX. MARKS: 15



COURSE NAME: Electrical Sciences

COURSE INSTRUCTORS: Prof. Rajiv Kumar, Dr. Harsh Sohal, Dr. Shweta Pandit, Dr. Salman Raju, Dr. Nishant Jain and Lt. Pragya Gupta

MAX. TIME: 1 Hour

**Note:** (a) All questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

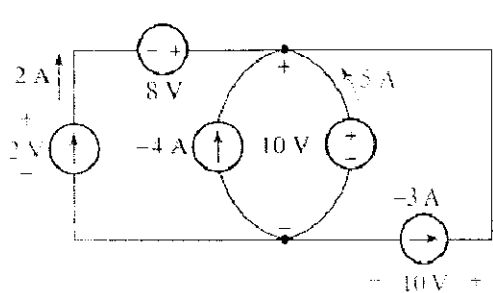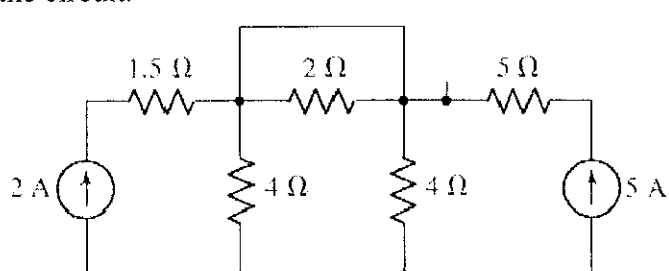Q.No	Question	CO	Marks
Q1	<p>Determine the power supplied by the leftmost element in the circuit of figure below.</p>  <p>Fig. 1.</p>		3
Q2	<p>Referring to the circuit depicted in Fig. 2, Redraw the circuit with effective circuit elements and then give the count of effective (a) nodes; (b) elements; (c) branches. In the circuit.</p>  <p>Fig. 2.</p>		3
Q3	<p>(a) In the circuit shown in Fig. 3, the resistor values are unknown, but the source is known to be supplying a current of 7 A to the rest of the circuit. Calculate the current labeled <math>i_2</math>.</p>	2 V	2 + 2 = 4

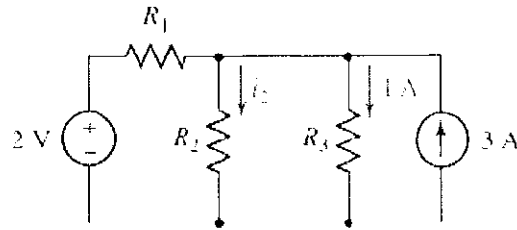


Fig. 3

(b) In the circuit of Fig. 4, it is determined that  $v_1 = 3\text{ V}$  and  $v_3 = 1.5\text{ V}$ . Calculate  $v_R$  and  $v_2$ .

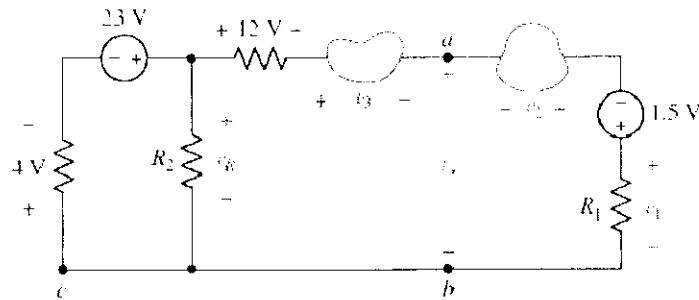


Fig. 4.

Q4 In the circuit of Fig. 5 below, determine the current labeled  $i$  with the assistance of nodal analysis techniques.

2

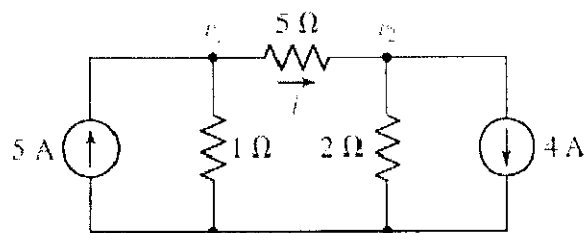


Fig. 5.

Q5 Employing the supermesh technique to best advantage, obtain numerical values for each of the mesh currents identified in the circuit depicted in Fig. 6.

3

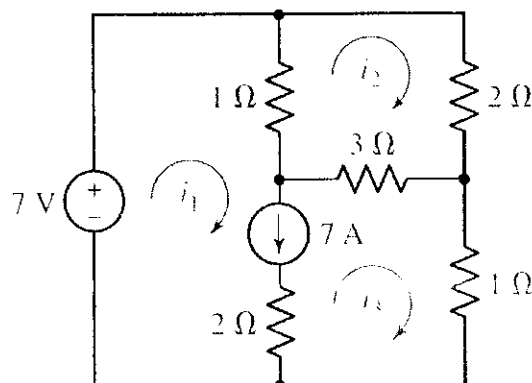


Fig. 6.