

COURSE CODE(CREDITS): 24B11EC211(4)/18B11EC211(4)



MAX. MARKS: 35





COURSE NAME: Basic Electrical Engineering/Electrical Sciences

COURSE INSTRUCTORS: RKU, HSL, SWT, NTJ, PRG, SRU

MAX. TIME: 2 Hours

Note: (a) All questions are compulsory. (b) The candidate is allowed to make suitable numeric assumptions wherever required for solving problems.

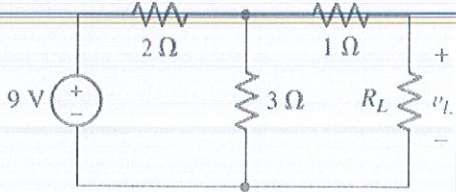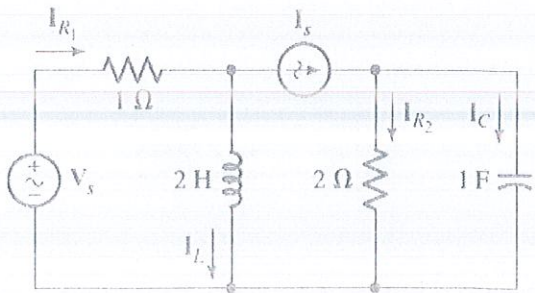Q.No	Question	CO	Marks
Q.1	<p>(a) Explain Source Transformation Theorem with an example.</p> <p>(b) Give the statement of Norton's Theorem. Mention the procedure to convert a circuit into a Norton's Equivalent circuit. Obtain the Norton equivalent of the network connected to R_L. Determine v_L for $R_L = 1, 3.5, 6.257$, and 9.8Ω.</p>	CO-2	2+5
			
Q.2	<p>(a) If the source v_s in circuit is equal to $4.53 \cos(0.333 \times 10^3 t + 30^\circ)$ V, (i) obtain i_s, i_L, and i_R at $t = 0$ assuming no transients are present; (ii) obtain an expression for $v_L(t)$ in terms of a single sinusoid, valid for $t > 0$, again assuming no transients are present.</p> <p>(b) In the circuit shown below, both sources operate at $\omega = 1$ rad/s. If $I_C = 2\angle 28^\circ$ A and $I_L = 3\angle 53^\circ$ A, calculate (i) I_s; (ii) V_s; (iii) $i_{R_1}(t)$.</p>	CO-3	4+3
			

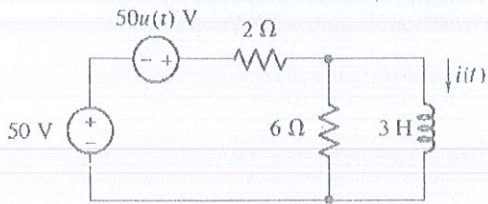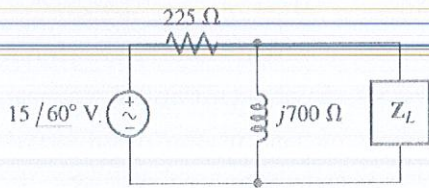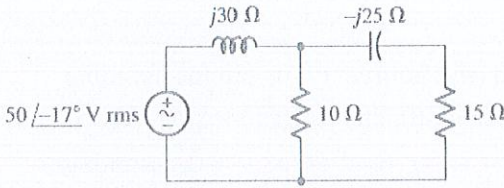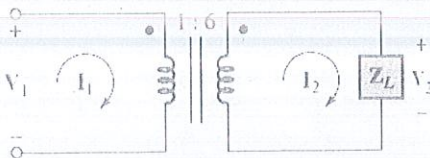Q.No	Question	CO	Marks
Q.3	<p>(a) Determine $i(t)$ for all values of time in the circuit.</p>  <p>(b) A parallel RLC circuit contains a $100\ \Omega$ resistor and has the parameter values $\alpha = 1000\ s^{-1}$ and $\omega_0 = 800\ \text{rad/s}$. Find (i) C; (ii) L; (iii) s_1 and s_2 (roots of the CE/AE).</p>	CO-4	4+3
Q.4	<p>(a) What load impedance Z_L will draw the maximum average power from the source shown below? Calculate the maximum average power supplied to the load.</p>  <p>(b) Calculate the complex power delivered to $15\ \Omega$ of the circuit, and determine the power factor of the source.</p> 	CO-4	3+4
Q.5	<p>(a) What is the significance of the dot convention in a transformer, and how does it help in determining the polarity of voltages?</p> <p>(b) What is self-inductance in a transformer winding? How is it different from mutual inductance?</p> <p>(c) Calculate I_2 and V_2 for the ideal transformer circuit shown below if $V_1 = 4\angle 32^\circ$ and $Z_L = 1 - j\ \Omega$.</p> 	CO-5	1+2+4