

53

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -1 EXAMINATION- 2025

B.Tech-I Semester (CSE (all branches)/IT/ECE/ECS/EEVLSI/CE)

COURSE CODE (CREDITS): 25B11EC111

MAX. MARKS: 15



COURSE NAME: BASIC ELECTRONICS

COURSE INSTRUCTORS: Prof. Rajiv Kumar, Prof. Shruti Jain, Dr. Harsh Sohal, Dr. Shweta Pandit, Dr. Salman Raju, Dr. Nishant Jain, Dr. Alok Kumar, Lt. Pragya Gupta.

MAX. TIME: 1 Hour

Note: (a) All questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems.

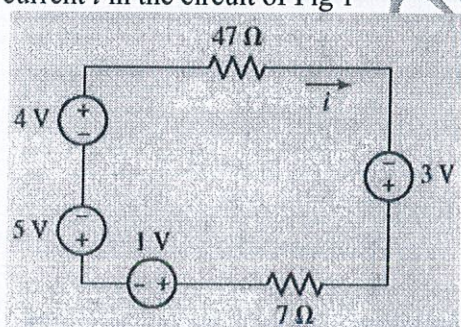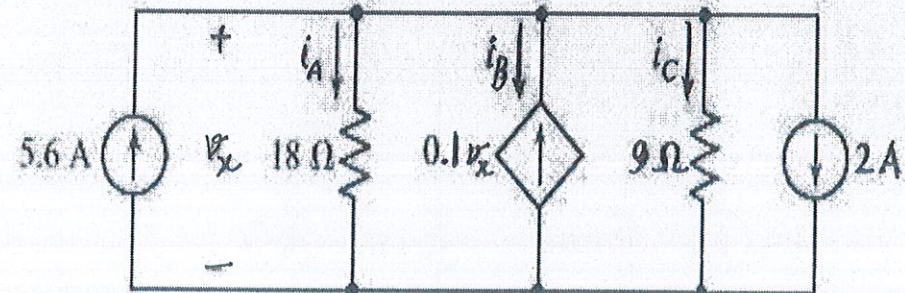Q.N o	Question	CO	Marks
Q1	<p>i. Determine the current i in the circuit of Fig 1 [2]</p>  <p>Fig 1</p> <p>ii. For the single-node-pair circuit of Fig. 2, find i_A, i_B, and i_C. [3]</p>  <p>Fig 2</p>	1	5
Q2	<p>i. With the help of nodal analysis, determine the voltage difference $v_1 - v_2$ in the circuit shown in Fig 3. [2]</p>	1	5

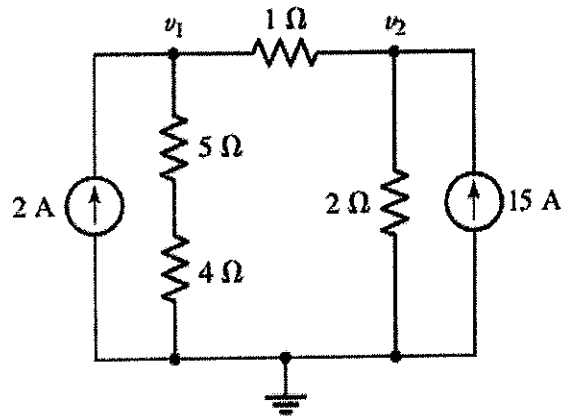


Fig 3

- ii. Using mesh analysis, determine the power (in watts) dissipated by the $4\ \Omega$ resistor in the circuit shown in Fig 4. [3]

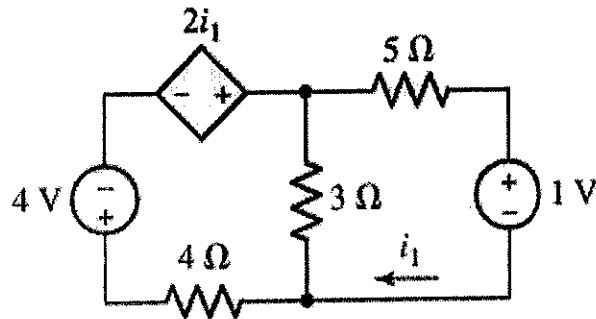


Fig 4

- Q3. i. Suppose you are designing an electronic system and need to connect a load resistor R_L to a given circuit. Determine load current using Norton's Theorem. Assume $R_L = 1\text{ k}\Omega$. [4]

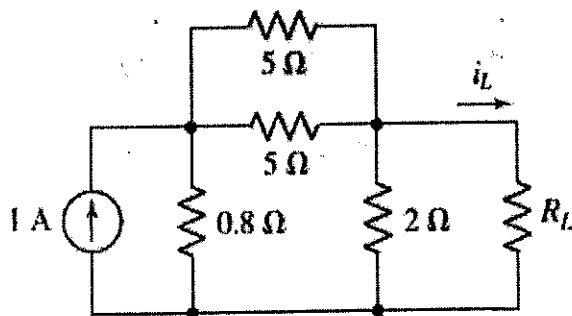


Fig 5

- ii. Convert the Norton's equivalent circuit obtained in Q 3 (i) to Thevenin's equivalent circuit using source transformation. [1]