

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT  
TEST -1 EXAMINATION- 2025

B.Tech-I Semester (CSE/IT/ECE/CE/BT/BI)

COURSE CODE (CREDITS): 25B11EC112 (4)

MAX. MARKS: 15




COURSE NAME: Basic Electronics for Life Sciences

COURSE INSTRUCTORS: Er. Munish Sood

MAX. TIME: 1 Hour

**Note:** (a) All questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

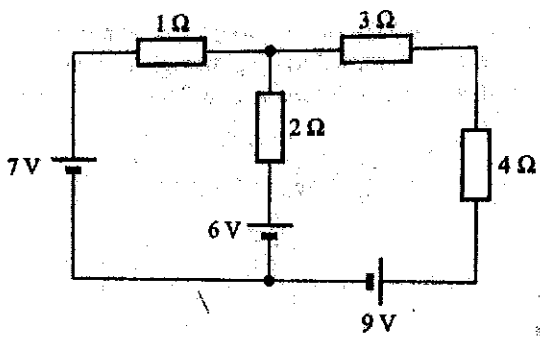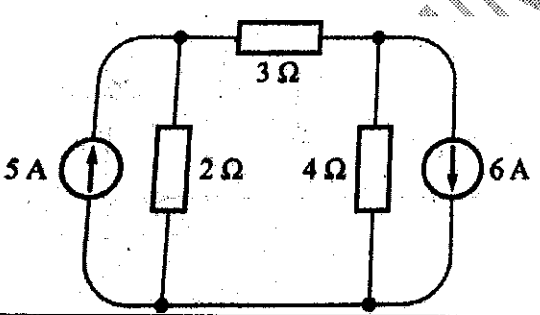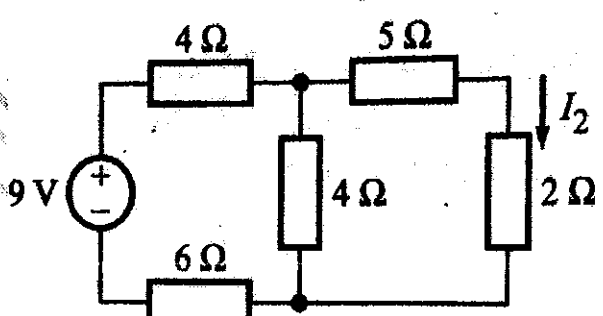
Q.No	Question	CO	Marks
Q1	<p>Using Mesh analysis determine the voltage across <math>2\ \Omega</math> resistor.</p> 	1	3
Q2	<p>Using Nodal analysis determine the voltage across <math>3\ \Omega</math> resistor.</p> 	1	3
Q3.	<p>Using Thevenin's theorem, calculate the current <math>I_2</math> through <math>2\ \Omega</math> resistor.</p> 	2	4

Q4.

Using Superposition theorem determine the current  $I_x$  for the given

2

5

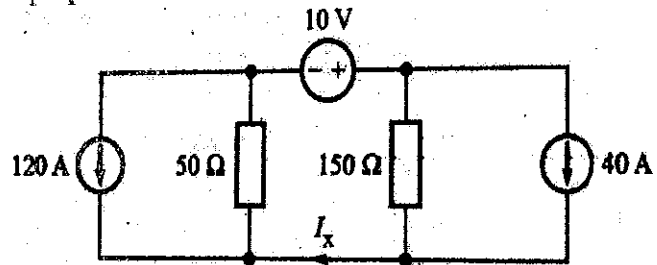

circuit.