

102

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -1 EXAMINATION- 2025

B.Tech-III Semester (ECE/ECS/EE VLSI)

COURSE CODE (CREDITS): 25B11EC313 (04) / 25B11EC314 (03)

MAX. MARKS: 15



COURSE NAME: Electronic Devices and Circuits / Electronic Devices



COURSE INSTRUCTORS: Dr. Shruti Jain

MAX. TIME: 1 Hour

Note: (a) All questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

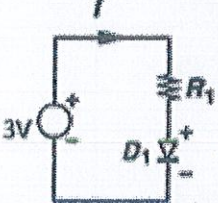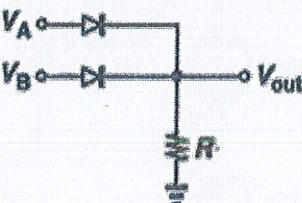Q.No	Question	CO	Marks
Q1	<p>i. The thermal voltage when the temperature is 25°C.</p> <p>ii. Voltage drops produced by a diode at forward bias in ideal diode model is equal to _____</p> <p>iii. What is the current <math>I</math> through the circuit (shown in Fig 1) if we consider diode in ideal diode model.</p> <div style="display: flex; justify-content: space-around; align-items: center;">   </div> <p style="text-align: center;">Fig 1                      Fig 2</p> <p>iv. What will be the voltage <math>V_{out}</math> (shown in Fig 2) if <math>V_A = 3V</math> and <math>V_B = -5V</math> and the diodes are ideal?</p> <p>v. The threshold voltage of a diode at Kailsah and Srilanka were found to be <math>V_1</math> and <math>V_2</math> respectively. Which of the following relations between <math>V_1</math> and <math>V_2</math> hold good?</p> <p>vi. A positive clipper using an ideal diode clip _____ of input signal.</p> <p>vii. Which circuit element is usually added in series with a diode in a clipper circuit?</p> <p>viii. For a half-wave rectifier, the average DC output voltage (without filter) is _____.</p> <p>ix. Sita is working on a rectifier circuit. Help her by stating the efficiency of a half-wave rectifier and a full-wave rectifier.</p> <p>x. A full-wave bridge rectifier is supplied from a transformer that gives an output of <math>V_{rms} = 12V</math> (secondary). Assume diodes are ideal. Find the DC output voltage.</p>	1	5

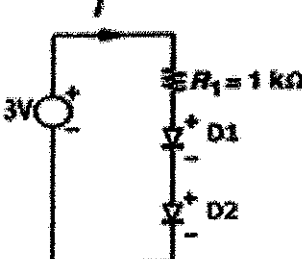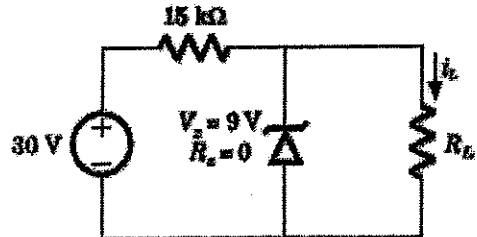Q2	<p>i. Calculate the reverse saturation current of a diode if the current at 0.2V forward bias is 0.1mA at a temperature of 25°C and the ideality factor is 1.5. [2]</p> <p>ii. Derive the equation [2]</p> <p>a) load line for a circuit consisting of a DC source, a series resistor, and a diode.</p> <p>b) <math>E_F = E_V + \frac{E_G}{2}</math> (terminologies define the same meaning)</p> <p>iii. Draw and explain the variation of diode capacitance with applied voltage (both forward and reverse bias regions) [1]</p>	1	5
Q3.	<p>i. Find current <math>I</math> through the circuit using shockley equation of diode. The terminal voltage of each diode is 0.6 V. Reverse saturation current is <math>10^{-12}</math>A. [2]</p> <div style="display: flex; justify-content: space-around; align-items: flex-end;"> <div style="text-align: center;">  <p>Fig 3</p> </div> <div style="text-align: center;">  <p>Fig 4</p> </div> </div> <p>ii. An <math>n</math>-type silicon semiconductor has <math>N_D = 5 \times 10^{17} \text{ cm}^{-3}</math> and <math>N_C = 2.8 \times 10^{19} \text{ cm}^{-3}</math>. Calculate the Fermi level shift from the conduction band. [1.5]</p> <p>iii. Find the maximum load current that can be drawn as shown in Fig 4. [1.5]</p>	1	5