

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -2 EXAMINATION- 2025

B.Tech-I Semester (CSE/IT/ECE/CE)

COURSE CODE (CREDITS): 25B11EC111 (4)

MAX. MARKS: 25

COURSE NAME: BASIC ELECTRONICS



MAX. TIME: 1 Hour 30 Min







COURSE INSTRUCTORS: RKU, SHR, HSL, SWT, SRU, ALK, NTJ, PRG

Note: (a) All questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

(c) Use of a scientific calculator is allowed.

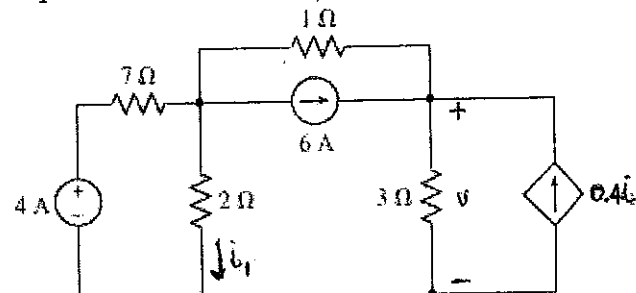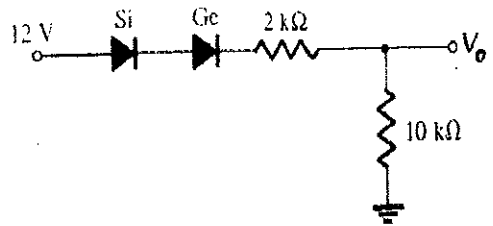Q.No	Question	CO	Marks
Q1	<p>a. Employ superposition to determine the individual contribution from each independent source to the voltage v as labeled in the circuit below.</p>  <p>b. Demonstrate that Superposition is not applicable for power dissipation across any element.</p>	3	[4]
Q2	<p>a. With the help of the circuit diagram and the diode's characteristic curve, explain the concepts of forward and reverse biasing of diodes.</p> <p>b. For the silicon diode, draw the circuit and its characteristic curve for the following equivalent circuits:</p> <ol style="list-style-type: none"> Piecewise linear equivalent circuit. Simplified equivalent circuit. Ideal equivalent circuit. 	2	[3]
Q3	<p>a. Explain the concept of a diode load line and its significance in analyzing diode circuits. Analyze the relationship between the load line and VI- characteristics of diode to identify the operating point (Q-point).</p> <p>b. Determine V_o for the circuit given on right side:</p> 	2	[2]
			[1]

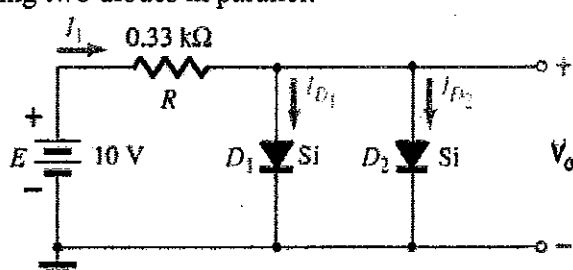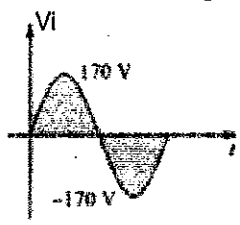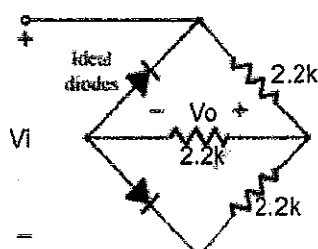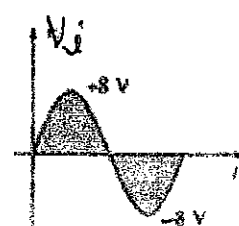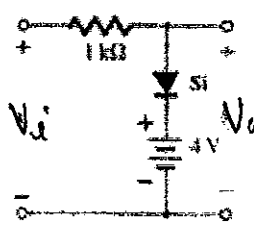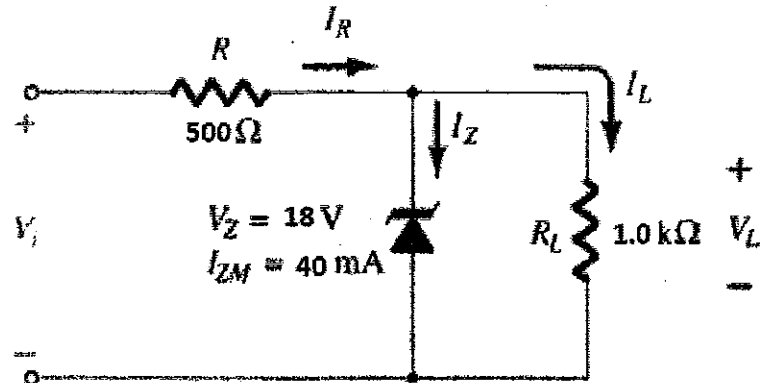	<p>c. Determine V_0, I_1, I_{D1}, and I_{D2} for the following parallel diode configuration. Analyze the circuit to provide the advantage of placing two diodes in parallel:</p> 		[2]
Q4	<p>a. Sketch the V_0 for the given circuit with a suitable explanation for the given sinusoidal input.</p>   <p>b. Sketch the V_0 for the given circuit with a suitable explanation for the given sinusoidal input.</p>  	2	[2.5]
Q5	<p>a. Determine the range of values of V_i that will maintain the Zener diode of Fig. shown below in the "on" state.</p> <p>b. Determine the maximum wattage rating of the zener diode.</p> 	2	[2+2] [1]