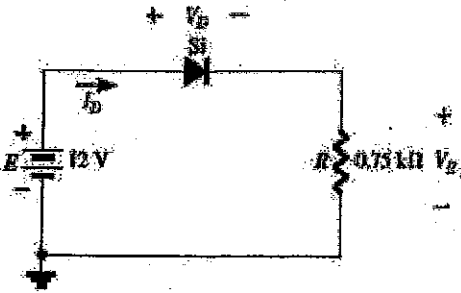
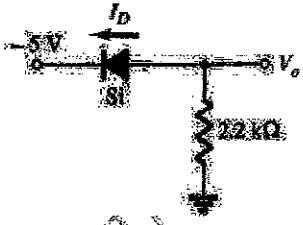
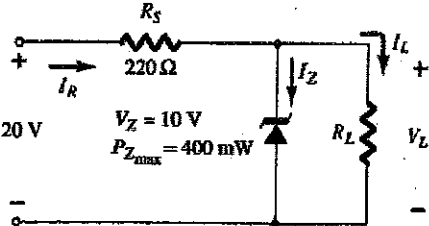


Q.No	Question	CO	Marks
Q.3	<p>A. Using the load-line analysis, determine I_D, V_D and V_R for the circuit using a conventional Si diode characteristic.</p>  <p>B. Determine the level of V_o for network using diode equivalent circuit in forward-bias condition.</p> 	CO-2	2+2
Q.4	What do you mean by rectification? Draw the circuit diagrams for full-wave rectifier and half-wave rectifier along with wave forms.	CO-3	4
Q.5	<p>Determine V_L, I_L, I_Z, and I_R for the network.</p> 	CO-3	4
Q.6	<p>Define/Explain the following terms in brief.</p> <ol style="list-style-type: none"> 1. Open Circuit and Short circuit 2. Linear and Non-linear devices 3. Minority and Majority Carriers 4. Conductors and Semiconductors 5. Ideal Diode and Practical Diode 	CO-3	5

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

MAKEUP EXAMINATION - NOVEMBER 2025

B.Tech-I Semester (CSE/ECE/IT/CE)



COURSE CODE(CREDITS): 25B11EC111(4)

MAX. MARKS: 25

COURSE NAME: Basic Electronics

COURSE INSTRUCTORS: RKU, SHR, HSL, SWT, SRU, NTJ, ALK, PRG MAX. TIME: 1hr. 30min

Note: (a) All questions are compulsory. (b) The candidate is allowed to make suitable numeric assumptions wherever required for solving problems. (c) Scientific Calculator is allowed.

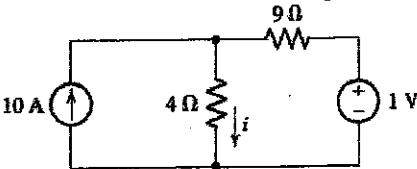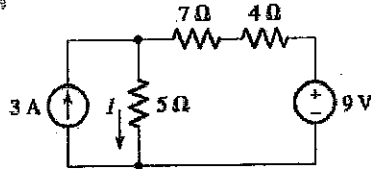Q.No	Question	CO	Marks
Q.1	<p>A. Use Superposition principle to find i in the circuit.</p>  <p>B. Determine the current labeled I in the circuit by converting it into a simple circuit consisting of a voltage source and a resistor along with 5Ω using Source Transformation.</p> 	CO-1	2+2
Q.2	<p>A. Given a diode current of 8 mA and $n = 1$, find I_s if the applied voltage is 0.5 V and the temperature is room temperature (25°C).</p> <p>B. Give the expressions for different resistance levels along with diagrams for a pn junction diode characteristic in forward bias region.</p>	CO-2	2+2