

**JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT**  
**Make-up Examination-Nov-2025**

COURSE CODE (CREDITS): 25B11EC112(4)

MAX. MARKS: 25

COURSE NAME: Basic Electronics for Life Sciences

COURSE INSTRUCTORS: Er. Munish Sood

MAX. TIME: 1 Hour 30 Minutes

**Note:** (a) All questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

(c) Scientific Calculators are allowed.

Q.No	Question	CO	Marks
Q1	<p>Determine <math>I</math>, <math>V_1</math>, <math>V_2</math> and <math>V_O</math> for the following network.</p>	2	5
Q2	<p>Determine <math>V_O</math>, <math>I_1</math>, <math>I_{D1}</math>, <math>I_{D2}</math> for the following network.</p>	2	5
Q3	<p>Determine <math>V_O</math> for the network.</p>	3	5
Q4	<p>Determine <math>V_O</math> for the following network.</p>	3	5

Q5	For the following network find $i_1, i_2$ and $v_3$ .	1	5

JUIT Make-up Examination-Nov-2025