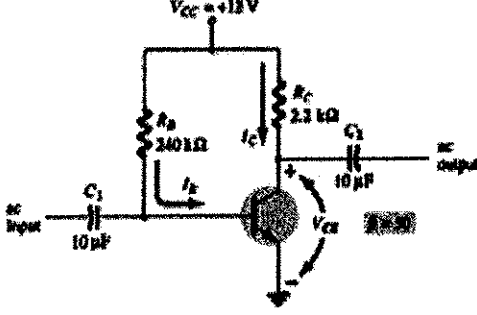


Note: (a) All questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

Q.No	Question	CO	Marks
Q1	<p>i. For a voltage divider biased NPN transistor <math>V_{CC} = 18\text{ V}</math>, <math>R_1 = 39\text{ k}\Omega</math>, <math>R_2 = 10\text{ k}\Omega</math>, <math>R_C = 3.3\text{ k}\Omega</math>, <math>R_E = 1\text{ k}\Omega</math>, <math>\beta = 150</math>, Find Q-point. What is the function of the emitter resistor <math>R_E</math>?</p> <p>ii. From the given circuit, using a silicon transistor, what is the value of <math>I_{BQ}</math> and <math>V_{CE}</math>?</p>  <p>Handwritten notes:  <math>R_C = 2.2\text{ k}\Omega</math>  <math>R_B = 240\text{ k}\Omega</math>  <math>\beta = 50</math>  <math>V_{CC} = 12\text{ V}</math></p>	2	2.5 + 2.5
Q2	<p>A microcontroller operates at 3.3 V, and is used to drive a 12 V DC motor through a power transistor. The motor draws a peak current of 1.5 A. The designer chooses an n-channel Enhancement MOSFET instead of a BJT.</p> <p>i. Why is a BJT not ideal for this switching application?          Explain why an enhancement MOSFET is suitable as a high-current switch. Write current equations for three regions.</p> <p>iii. What is the role of threshold voltage <math>V_{th}</math> in deciding MOSFET turn-on?          Explain all conditions.</p> <p>iv. How does using a MOSFET improve efficiency and reduce heating?</p> <p>v. Write the equation of <math>V_{DS}</math> considering the circuit as voltage divider biasing.</p>	3	1 × 5
Q3	<p>i. For an n-channel self-bias JFET : <math>I_{DSS} = 12\text{ mA}</math>, <math>V_P = -4\text{ V}</math>, <math>R_S = 1\text{ k}\Omega</math>. Find <math>I_D</math> and <math>V_{GS}</math></p> <p>ii. For a given n-MOSFET <math>V_{DD} = 10\text{ V}</math>, <math>R_D = 2.2\text{ k}\Omega</math>, <math>V_{GS} = 4\text{ V}</math>, <math>V_{TH} = 2\text{ V}</math>, <math>k = 1\text{ mA/V}^2</math>. Find <math>I_D</math> and <math>V_{DS}</math>.</p>	4	2 + 1 + 1 + 1

	<p>iii. In a CS amplifier, given that <math>r_{ds} = 0.5M\Omega</math> and <math>g_m = 5m\Omega^{-1}</math>, the load is <math>10k\Omega</math>, source resistance is <math>44k\Omega</math>. Calculate the internal amplification factor for the small signal model.</p> <p>iv. For an n-channel JFET with <math>I_{DSS} = 12mA</math> and <math>V_P = -3V</math>. Find the small-signal transconductance <math>g_m</math> at <math>V_{GS} = -1V</math>.</p>		
Q4	<p>i. The JFET with <math>g_m \approx 5.33mS</math> at the bias point is used in a common-source amplifier with drain resistor <math>R_D = 10k\Omega</math>. The source is bypassed (source at AC ground). Estimate the small-signal voltage gain <math>A_v</math> (neglect <math>r_o</math>).</p> <p>ii. Explain the difference between Low-frequency response of BJT amplifier and Low-frequency response of FET amplifier. Also, explain her High frequency transistor models and small signal models.</p>	5	1.5 + 3.5
Q5	<p>i. A sensor output very small voltage signal and need extremely high input impedance at the amplifier stage. Which FET type would you select and why?</p> <p>ii. In a battery-powered IoT device, energy efficiency is critical. Explain why MOSFETs are used in the on/off control stage instead of BJTs.</p> <p>iii. A mixer circuit in RF uses a JFET as a voltage-controlled element. Explain how the JFET's pinch-off behaviour contributes to mixing.</p> <p>iv. What are the two intercepts of a DC load line for JFET?</p> <p>v. Fig shows the transfer characteristics of JFET. Write the equation for drain current.</p>	5	1 × 5
Q6	<p>i. What happens to <math>g_m</math> if <math>I_D</math> increases? Explain with equation.</p> <p>ii. The datasheet of a JFET gives following information <math>I_{DSS} = 3mA</math>, <math>V_P = -6V</math>, <math>g_{m0} = 5000\mu S</math>. Determine the transconductance for <math>V_{GS} = -4V</math>. Evaluate <math>R_S</math>.</p> <p>iii. What are the three main frequency regions of a single-stage amplifier? Which region shows maximum flat gain? How does cascading amplifiers affect overall gain?</p>	6	1 + 2 + 2
Q7	Shyam is working on his major project. He got confused in rectifiers and clippers. Differentiate between rectifiers, and clippers. Explain the purpose of each circuit with suitable examples and waveforms.	1	5