

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -3 EXAMINATION- 2025

B.Tech-V Semester (ECE)

COURSE CODE (CREDITS):18B1WEC534

MAX. MARKS: 35

COURSE NAME: NETWORK ANALYSIS AND SYNTHESIS

COURSE INSTRUCTORS: Dr Rajiv Kumar

MAX. TIME: 2 Hours

Note: (a) All SIX questions are compulsory.

(b) The candidate is allowed to make Suitable numeric assumptions wherever required for solving problems

(c) Students are allowed to use non-programmable scientific calculator

Q.No	Question	CO	Marks
Q1	<p>A) What do you mean by Hurwitz polynomials? What are the necessary conditions for a polynomial to be Hurwitz?</p> <p>B) Using the Routh–Hurwitz criterion, check whether the following polynomials are Hurwitz or not:</p> <ol style="list-style-type: none"> $P_1(s) = s^3 - 2s^2 + 3s + 1$ $P_2(s) = s^3 + 6s^2 + 11s + 6$ $P_3(s) = 2s^4 + 8s^3 + 12s^2 + 10s + 3$ 	CO-4	3+3=6
Q2	<p>Derive the conditions under which following biquadratic function is positive real (PR).</p> $F(s) = \frac{s^2 + a_1 s + a_0}{s^2 + b_1 s + b_0}$ <p>Show all necessary steps and state the final PR conditions in terms of the coefficients.</p>	CO-3	5
Q3	<p>In the following two cases, synthesize a passive R–L–C network that realizes the impedances:</p> $Z_1(s) = \frac{s^2 + 2s + 6}{s(s + 3)}$ $Z_2(s) = \frac{6s^3 + 3s^2 + 3s + 1}{6s^3 + 3s}$ <p>(a) Prove that both impedances are positive-real.</p> <p>(b) Draw the final circuit and give the numerical element values.</p>	CO-1	3+3=6

Q4	<p>A) What is meant by an L-C driving-point impedance? Explain with an example. How do the properties of L-C driving-point impedances differ from those of R-L or R-C impedances?</p> <p>B) Synthesize the L-C driving-point impedance</p> $Z(s) = \frac{s^4 + 42s^2 + 4s}{s^5 + 18s^3 + 48s}$	CO-3	3+3=6
Q5	<p>A) What is a state transition matrix (STM)? State and explain any four important properties of the STM, $\Phi(t)$.</p> <p>B) Define $\Phi(t)$ for a linear time-invariant system with following 3×3 state matrix:</p> $A = \begin{bmatrix} 0 & 1 & 0 \\ 0 & 0 & 1 \\ -6 & -11 & -6 \end{bmatrix}$	CO-3	3+3=6
Q6	<p>A) Define the A-parameters of a two-port network and explain their physical significance.</p> <p>B) You are given the open-circuit impedance (Z) matrix of a two-port network:</p> $Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$ <p>Determine the condition whether the network is symmetrical or reciprocal.</p>	CO-2	3+3=6