

6

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

ACCELERATED SEMESTER

MID-TERM EXAMINATION-2026

B.Tech-VII Semester (CSE/IT/BT/BI/CE)

COURSE CODE (CREDITS): 20B1WEC734 (3)



MAX. MARKS: 50

COURSE NAME: Digital Systems

COURSE INSTRUCTOR: Dr. Pardeep Garg

MAX. TIME: 2 Hours

*Note: (a) All questions are compulsory. (b) The candidate is allowed to make suitable numeric assumptions wherever required for solving problems. (c) A non-programmable calculator is allowed.*

  Q. No	Question	CO	Marks
Q1	Each of the following arithmetic operations is correct in at least one number system. Determine the possible base in each case: i) $\frac{41}{3} = 13$ ii) $\sqrt{41} = 5$	CO-1	2.5+2.5=5
Q2	Convert $(987)_{10}$ into gray code, hexadecimal equivalent, and 2's complement formats.	CO-1	2*3=6
Q3	The message <b>(0011011)</b> coded in the 7-bit Hamming code is transmitted through a noisy channel. Decode the message assuming that at most a single error occurred in the code-word. Compute the error location and find the corrected code-word.	CO-1	5
Q4	For the two-input NAND gate operating as a negative OR gate (Fig. 1(a)), sketch the output waveform when the input waveforms A and B are as depicted in Fig. 1(b).  Fig. 1(a)  Fig. 1(b)	CO-1	4
Q5	Write down the minimized expression by solving the following expression using K-map and implement the minimized expression using AOI logic and universal gates: $f = \sum m(0, 1, 4, 5, 6, 7, 9, 11, 15) + d(10, 14)$	CO-1	7
Q6	Design a Full Adder using 3:8 decoder.	CO-3	5
Q7	Design a 32:1 multiplexer using two 16:1 multiplexer and one 2:1 multiplexer (in one circuit); discuss its working along with the truth-table.	CO-3	8
Q8	Draw the logic diagram of 4-bit SISO, SIPO, PISO, and PIPO Shift Registers (using D flip-flops).	CO-2	2.5*4=10