

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST-2 EXAMINATION-MARCH-2026

B.Tech- IV<sup>th</sup> Semester (CSE/IT)

COURSE CODE (CREDITS): 25B11CI411 (3)

MAX. MARKS: 25

COURSE NAME: Digital Systems and Computer Organization

COURSE INSTRUCTORS: SWT (Coordinator), EMJ, PDG, ALK, NTJ, MSD

MAX. TIME: 1.5 Hours

Note: (a) All questions are compulsory. (b) The candidate is allowed to make suitable numeric assumptions wherever required for solving problems. (c) Calculator is not allowed.

Q. No	Question	CO	Marks
Q1	A combinational circuit has to be designed in such a way that it provides the 2's complement as output for 4-bit binary number as input. Show the following: i) Truth-Table ii) Boolean expression for the output variables	CO-2	2+2=4
Q2	A 2-bit magnitude comparator for 2 inputs (A and B having bits A <sub>0</sub> , A <sub>1</sub> , and B <sub>0</sub> , B <sub>1</sub> respectively) has to be designed. Obtain the following: i) Boolean expression for the output variables ii) Show the logic circuit	CO-2	1.5+1.5=3
Q3	a) Implement the 24:1 MUX using 8:1 MUXs only. Clearly mention on the diagram which select line is the MSB and which select line is the LSB. b) Design a 2-input Ex-OR gate using one 2:1 MUX.	CO-2 CO-2	2 1
Q4	The waveform as shown in figure 1 is applied to (a) a positive-edge triggered J-K flip-flop, (b) a negative edge-triggered J-K flip-flop. Draw the output waveform in each case.	CO-3	1.5+1.5=3
	<p style="text-align: center;">Figure 1</p>		
Q5	Convert J-K flip flop to S-R flip flop using conversion table, excitation table and Karnaugh Map.	CO-2	4
Q6	Design a 4-bit asynchronous decade counter (MOD-10 counter)	CO-3	3+2=5

	<p>(a) Draw the complete logic circuit diagram showing all flip-flop connections and the asynchronous reset logic.</p> <p>(b) Draw the timing diagram for one complete counting cycle (from 0000 to 1001 and back to 0000), clearly showing the clock input and the four output waveforms <math>Q_3</math> <math>Q_2</math> <math>Q_1</math> <math>Q_0</math>. Label all transitions and indicate the reset pulse.</p>		
Q7	<p>Write short note on the following:</p> <p>a) The significance of asynchronous inputs (Preset and Clear) with truth-table.</p> <p>b) Differentiate between combinational and sequential circuits.</p> <p>c) Compare and contrast between latch and flip-flop.</p>	CO-3	3*1=3

UNIT TEST 2 EXAMINATION - MARCH 2026