

## JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

## TEST -2 EXAMINATION - 2022

## B.Tech. VIII Semester ( ECE )

COURSE CODE: 19B1WEC831

MAX. MARKS: 25

COURSE NAME: DIGITAL CMOS ICs

COURSE CREDITS: 03

MAX. TIME: 1 Hour 30 Min

**Note:** All questions are compulsory. Marks are indicated against each question in square brackets.

1. In logic design, complex gates such as AOI and OAI are often used to combine the functions of several gates into a single gate, thus reducing the chip area and parasitic of

the circuit. Consider OAI32 whose logic function is  $Z = \overline{(A+B+C)}(D+E)$ .

- Draw the full CMOS circuit diagram
  - Draw the domino CMOS circuit diagram which implements Z. [5]
2. Evaluate the optimum stage effort for the logic cascade as shown in Fig 1. Assume symmetric gates with  $r = 2.5$ . [5]

 


Fig 1

S	R	Q	$\bar{Q}$
0	1	1	0
1	0	0	1
1	1	Q	$\bar{Q}$

Fig .2

- Design the circuit using CMOS logic for Fig 2. [5]
- Geeta wants to draw CMOS D latch using transmission gates. Help her in drawing the circuit. Also, explain the circuit. [5]
- Draw and explain the Sense amplifier-based cross-coupled latch.
  - Shyam wants to remove the erroneous evaluation problem from the circuit. Which circuit he will use to remove this problem? [2.5 + 2.5]