

Dr. Meenakshi Sood. (ECE)

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT  
END TERM TEST  
SUMMER SEMESTER - JUNE 2016  
B.Tech/ IV Semester

COURSE CODE: 10B11EC401

MAX. MARKS: 50

COURSE NAME: DIGITAL ELECTRONICS

COURSE CREDITS: 3

MAX. TIME: 2 Hrs

---

*Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.*

---

1. Convert JK flip flop to SR flip flop. [7 Marks]
2. Differentiate between Ring counter and Johnson counter. [6 Marks]
3. Design a 4 bit BCD synchronous counter. [7 Marks]
4. With help of a suitable diagram explain the working of 555 timer as an astable multivibrator. [7 Marks]
5. Explain the working of a bidirectional shift register with the help of suitable diagram. [ 8 Marks]
6. How does TTL NAND gate work? Explain with the help of suitable diagram. [7 Marks]
7. Design a counter using JK flip flop that goes through a repeated sequence as 0,3,5,7,9,12,13. [8 marks]

\*\*\*\*\*