

JAYPEE UNIVERSITY OF INFORMATRION TECHNOLOGY, WAKNAGHAT

TEST -1 EXAMINATION, September-2016

B.Tech 1st Semester (ECE, CSE, IT & CE)

COURSE CODE: 10B11EC111

MAX. MARKS: 15

COURSE NAME: Electrical Circuit Analysis

COURSE CREDITS: 04

MAX. TIME: 1 HR

Note: All questions are compulsory; Carrying of mobile phone during examination will be treated as case of unfair means.

Q1. Find the condition when the circuit current is maximum in the circuit given in figure 1.

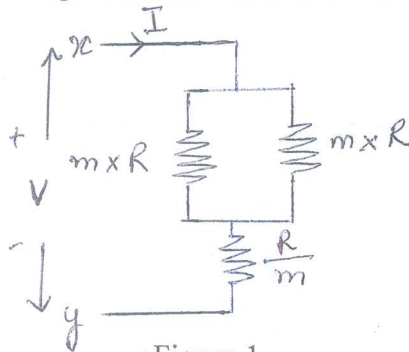


Figure 1

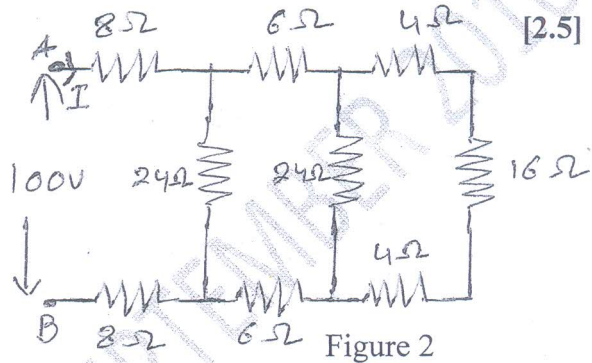


Figure 2

Q2. a) In the circuit shown in figure 2 determine a) the total current and b) the power delivered to the 16Ω resistance. [1.5+1.5]

b) Determine the voltage drop across 10Ω resistance in the circuit as shown in figure 3.

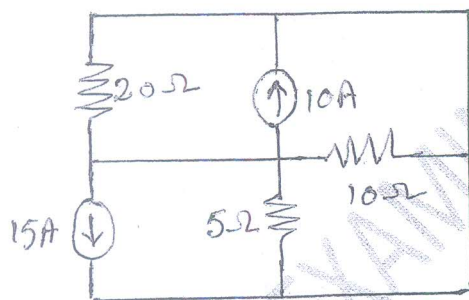


Figure 3

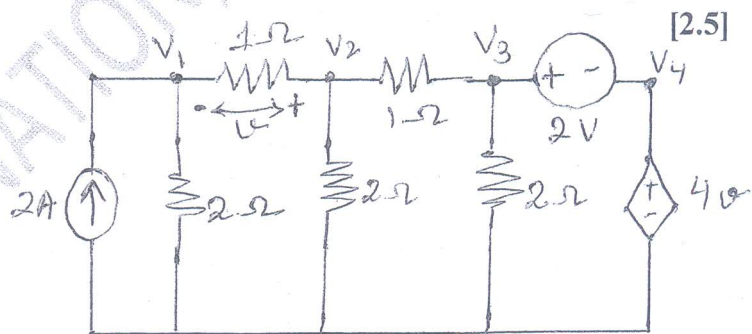


Figure 4

Q3 a) In the network shown in figure 4, find the voltages V_1 , V_2 , V_3 and V_4 using nodal analysis. [4]

b) Using mesh analysis, find the currents I_1 , I_2 and I_3 in figure 5. [3]

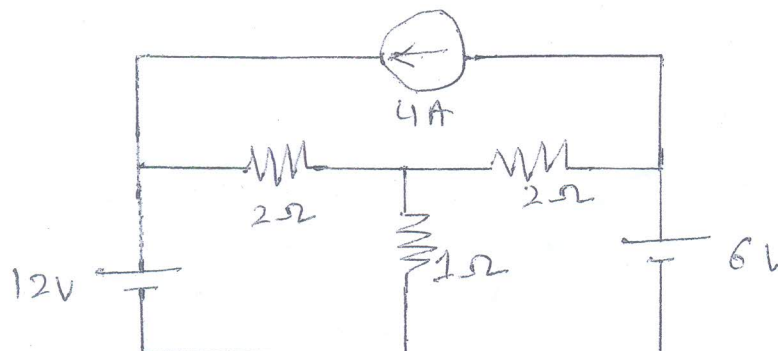


Figure 5