

## JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

## MAKEUP EXAMINATION- 2016

## B.Tech VI Semester

COURSE CODE: 11B1WEC611

MAX. MARKS: 25

COURSE NAME: Power Electronics

COURSE CREDITS: IV

MAX. TIME: 1Hr 30 Min

*Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.*

Q1. Using circuit diagram and wave shapes explain the working of single phase full converter feeding RLE load. A single phase 230V, 1kW load is connected across 1- phase 220V, 50Hz supply through an SCR. For firing angle delay of  $90^\circ$ , calculate the power absorbed in the heater element. [5]


Q2. Draw equivalent circuit diagram for UJT and explain how this device works. Also derive the expression for frequency of oscillation for UJT relaxation oscillator. [5]

Q3. For a two transistor model of thyristor, following data is given,

- i) Current gain for npn transistor is 0.5
- ii) Current gain for pnp transistor is 0.4

Calculate the value of minimum gate current, if anode current of value 20A is required. [5]

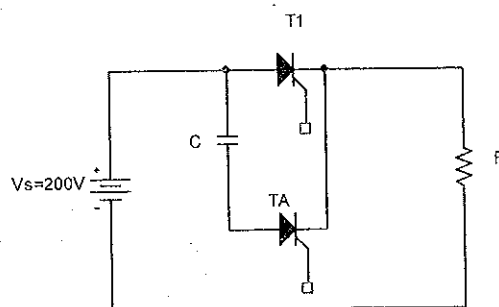Q4. For the circuit shown in figure 2, identify the type of commutation. If capacitor is initially charged to  $V_s$  with polarity as shown, find the circuit turn off time for the main thyristor in case  $C = 10\mu\text{F}$ ,  $R=5\Omega$ , and  $V_s= 200\text{V}$ .



[5]

Q5. What is the effect of unequal voltage distribution across SCR strings during their turn on and turn off process? Suggest methods to minimize this effect. [5]