

Note: All questions are compulsory.

1. a) Find the midpoint voltage for the circuit shown in Fig 1

[2.5]

 


Fig 1

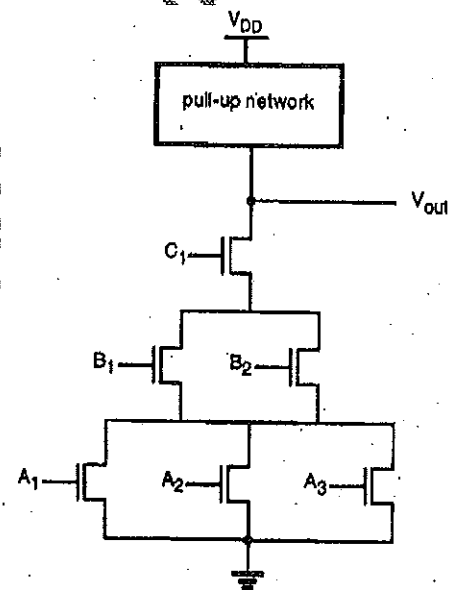


Fig 2

- b) A CMOS NOR<sub>2</sub> gate is designed using  $n$ MOS with a value of  $k_n$  and  $p$ MOS by  $k_p$ . MOS aspect ratios are 6 and 8 respectively. Find the value of  $V_{IH}$  in terms of  $V_{out}$  for the case of simultaneous switching if  $V_{DD} = 3.3V$ ,  $V_{Tn} = 0.65V$ ,  $V_{Tp} = -0.80V$ ,  $k_n = 150\mu A/V^2$ ,  $k_p = 62\mu A/V^2$ . [2.5]

2. Consider the circuit diagram given in Fig 2.

- a) Determine the logic function  $F$ . Find the equivalent  $n$ MOS inverter circuit for simultaneous switching of all input of Fig 2, assuming that  $(W/L)_n = 12$  for all  $n$ -mos transistor. [2]

- b) The inverter is biased at  $5V$ . The threshold voltages are  $V_{TOD} = 1V$ ,  $V_{TOL} = 2V$ ,  $K_n = 25\mu A/V^2$ ,  $\gamma = 0.4V^{1/2}$ ,  $|2\phi_f| = 0.5V$ . Design the inverter such that maximum power dissipation is  $400\mu W$  for output voltage is  $0.4V$ . Assume Pull up network as Saturated Load Inverter. [3]

3. a) A  $p$ -channel transistor for which  $|V_{th}| = 1.2V$  and  $|V_A| = 40V$  operates in saturation with  $|V_{GS}| = 2V$  and  $|V_{DS}| = 5V$ , and  $i_D = 5mA$ . Find the corresponding signed values for  $V_{SG}$ ,  $V_{SD}$ ,  $\lambda$ ,  $k_p$  (W/L). [0.5 + 0.5 + 0.5 + 1 = 2.5]
- b) A particular enhancement MOSFET for which  $V_{th} = 0.8V$  and  $k_n$  (W/L) =  $0.1mA/V^2$  is to be operated in the saturation region. If  $I_d$  is to be 0.2 mA, find the minimum required  $V_{DS}$ . [1.5]
- c) For an  $n$ -mOS transistor for which  $V_{th} = 1V$ , operating with  $V_{GS}$  in the range of 1.25V to 5V, what is the largest value of  $V_{DS}$  for which the channel remains continuous? [1]
4. In the inverter circuit, what is meant by  $Z_{P,U}$  and  $Z_{P,D}$ ? What are pass transistors? Derive  $Z_{pu}$  to  $Z_{pd}$  ratio for an  $n$ MOS inverter driven through one or more series pass transistors. [1 + 1 + 3 = 5]
5. Explain the different steps of fabrication of  $n$  - depletion type IGFET. [5]
6. Consider the following parameters for  $n$ - channel enhancement type MOSFET having linearly graded junction profile. Substrate doping =  $3 \times 10^{12} cm^{-3}$ , Source/Drain doping =  $1 \times 10^{19} cm^{-3}$ , Sidewall (P+) doping =  $2 \times 10^{22} m^{-3}$ , gate oxide thickness = 40 nm, junction depth = 1.2  $\mu m$ , length of drain = 10  $\mu m$ , width = 5  $\mu m$ , gate drain overlap length = 0.25  $\mu m$ ,  $m_{sw} = 0.5$ . Both the source and drain diffusion regions are surrounded by P+ channel stop implant. If drain voltage changes from 2.5 V to 5 V. Find drain substrate diffusion capacitance. [5]
7. Draw the stick diagram of Sum Function of Full Adder using CMOS logic. [2 + 3 = 5]

JUIT-3 EXAMINATIONS, JUNE 2016