

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT
 SUMMER SEMESTER (JULY 2016)- B-Tech
 END TERM EXAM

COURSE CODE: 10B11EC312
 COURSE NAME: Analogue Electronics
 COURSE CREDITS: 4

MAX. MARKS: 50
 MAX.TIME: 2 HRS

- Q1. a)** Elaborate the RC coupled amplifiers and draw its frequency response curve. (6)
- b)** Three identical cascaded stages have an overall upper 3-dB frequency of 100 kHz and a lower 3-dB frequency of 25 kHz. Determine f_L and f_H for each stage, assuming non interactive stages. (4)
- Q2. a)** Draw and explain the working of R-C phase shift oscillator and also derive an expression for its frequency of oscillations. (6)
- b)** Explain the push pull amplifiers and their advantages (4)
- Q3. a)** What are feedback amplifiers. Derive the gain of a negative feedback amplifier. (6)
- b)** To an amplifier with a gain of 60 dB, a negative feedback of $\beta = 0.006$ is applied. What will be the percentage change in the overall gain of the feedback amplifier if the internal gain of the amplifier reduces by 3 %. (4)
- Q4. a)** What are oscillators and derive the condition of Barkhusan for oscillations in electronic systems? (6)
- b)** Figure 1 shows the tuned circuit used in a Hartley oscillator, with $L_1 = 1 \mu\text{H}$, $L_2 = 0.2 \mu\text{H}$, and $C = 1000 \text{ pF}$. (i) What is its frequency of oscillation ? (ii) What is the feedback factor β ? (iii) For the oscillator to start, what is the minimum value of gain A ? (4)

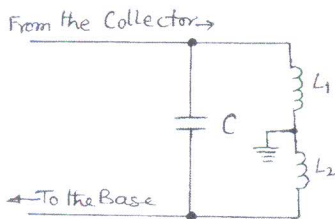


Fig 1

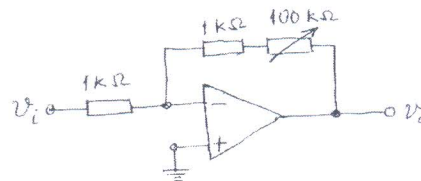


Fig 2

- Q5. a)** What is an ideal op-amp and discuss various applications of op-amp. (6)
- b)** The adjustable resistor of Fig.2 can be varied from 0 to 100 kΩ. Calculate the minimum and maximum closed-loop voltage gain. (4)