

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -3 EXAMINATION- 2021

B.Tech. ECE/CSE/IT 3rd Semester

COURSE CODE: 18B11EC312/10B11EC401

MAX. MARKS: 35

COURSE NAME: DIGITAL ELECTRONICS AND LOGIC DESIGN/ DIGITAL ELECTRONICS

COURSE CREDITS: 04

MAX. TIME: 2 Hours

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

1.

- i. Write the excitation table for JK flip flop.
- ii. Write the characteristic table for T flip flop.
- iii. Draw Active high SR latch.
- iv. What do you mean by edge triggering? Explain with the help of clock.
- v. Which flip flop is used to design Shift registers?
- vi. The complemented output of last flip flop is connected to input of first flip flop. Name and draw 2 bit circuit.
- vii. Name the sequential circuit given in Figure 1. [7 × 1 = 7]

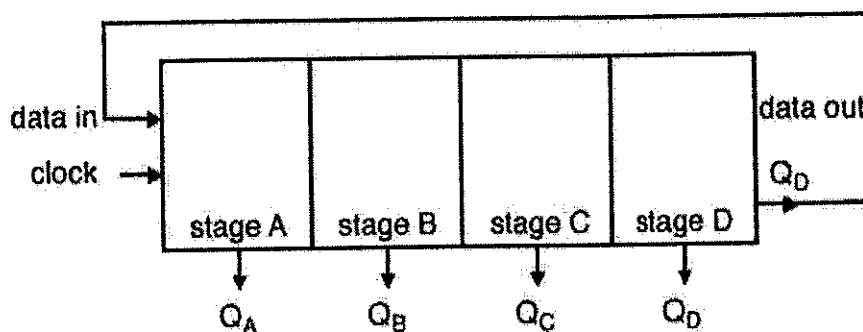


Figure 1

2. Design a circuit for conversion of D to JK flip flop. [4]

3. How many flip-flops are required to design MOD-13 up binary counter? Design the circuit in Asynchronous mode with timing diagram. [5]

4. Vinay just learned how a three-bit synchronous binary counter works, and he is excited about building his own. He does so, and the circuit works perfectly. Draw the circuit which Vinay has designed assuming T flip flop. [6]

5. Design how a shift register circuit could be built from D-type flip-flops with the ability to shift data either to the right or to the left, on command. [6]
6. For the state diagram given in Figure 2, design the sequential circuit using D flip flop. [7]

 


Figure 2

JUT TEST-3 EXAMINATION-DEC