

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -1 EXAMINATIONS-2022

B.Tech-II Semester (CE)

COURSE CODE (CREDITS): 18B11EC211 (4)

MAX. MARKS: 15

COURSE NAME: ELECTRICAL SCIENCE


COURSE INSTRUCTORS: ANUJ KUMAR MAURYA

MAX. TIME: 1 Hour


Note: All questions are compulsory. Marks are indicated against each question in square brackets.

- Q1. (a) What do you understand by active and passive component? [CO1] [1]
 (b) Explain voltage dividing and current dividing rule in electric circuits. [CO2] [2]

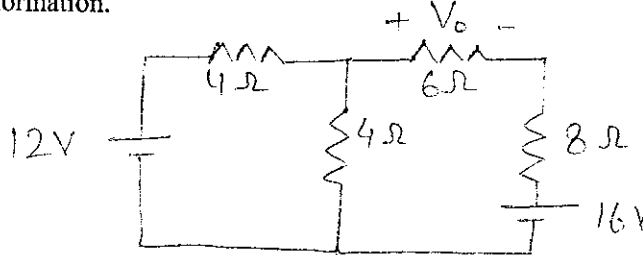- Q2. What is source transformation? Solve following circuit to find the value of V_0 using source transformation. [CO1, CO2] [3]



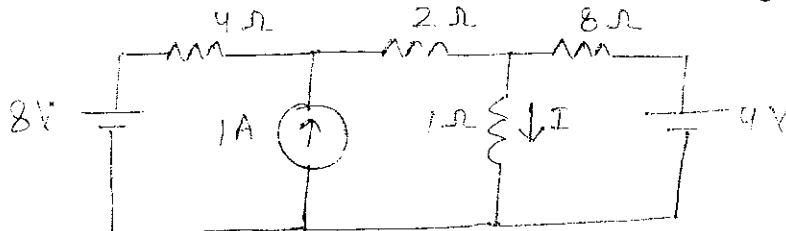- Q3. Define superposition principle and apply it to get the value of I in following circuit. [CO2, CO3] [3]



- Q4. What do you understand by star-delta connection? Develop the relation between different components of star-delta connection. [CO1, CO2] [3]

- Q5. Using Norton's theorem, find the current through A-B in the following circuit. [CO2, CO3] [3]

