
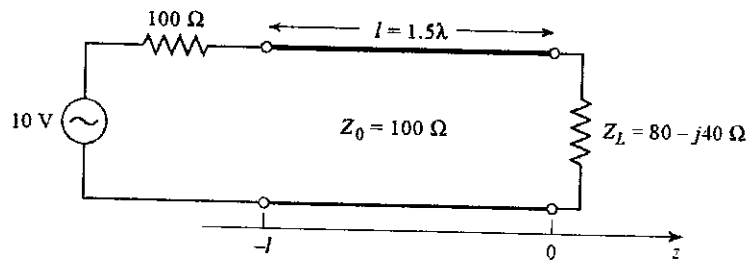


Note: All questions are compulsory. Marks are indicated against each question in square brackets.

- Derive an expression for the voltage on a transmission line using the distributed equivalent circuit of the transmission line. [4 marks] [CO-4]
- A generator is connected to a transmission line as shown in the accompanying figure. Find the reflection coefficient at the load, VSWR at the input, input impedance looking towards the load at $z = -l$. (Solve this problem without using the Smith chart). [3 marks] [CO-3]

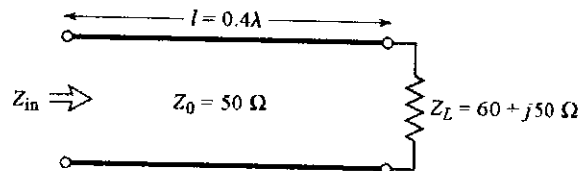

- Using the Smith Chart, design two lossless L -section matching circuits to match a load of $Z_L = 150 - j200 \Omega$ to a transmission line of 100Ω characteristic impedance at 3 GHz. [4marks] [CO-4]
- Derive the expression for VSWR in terms of the reflection coefficient. For the given circuit below, determine the distance from the load to the first voltage maximum. [2marks] [CO-3]



- Define/Explain the following. [2 marks] [CO-1 and CO-2]
 - Quarter wave transformer
 - Electrical length and physical length
 - Gauss law in point form and integral form
 - Insertion loss and Return loss

Smith Chart

