

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

Marks

Q1. (a) Find the nodal voltages of the circuit shown in Fig.1(a). [CO-1]

3

 


Fig. 1(a)

(b) If $V_1=10\text{ V}$, $V_2 = 15\text{ V}$, $R_1=4\Omega$, and $R_2=6\Omega$ in the circuit shown in Fig.1(b)
Find the Thevenin equivalent for the network to the left of terminals a,b.[CO-1]

2

 


Fig. 1(b)

Q2. (a) In the circuit shown in fig. 2 (a), a silicon diode with knee voltage 0.7 V is used.
The dynamic resistance of the diode in forward bias may assumed to be zero. [CO-2]

3

 


Fig. 2(a)

- (i) If $V_{DD} = 5\text{ V}$, what should be the value of R to establish a current of 5 mA in the Circuit?
- (ii) Determine the power dissipated in the resistance R and in the diode D , when a current of 5 mA flows in the circuit at $V_{DD} = 6\text{ V}$.

- (b) The current flowing in a PN junction diode at room temperature is 200 nA , when a large reverse bias is applied. Calculate the current through the diode when 0.1 V forward bias is applied. [CO-2] 2

- Q3. (a) Draw a typical common base output characteristics of a pnp transistor and indicate cutoff, active & saturation regions. [CO-3] 2

- (b) For a certain BJT, $\beta = 50$, $I_{CEO} = 3\text{ }\mu\text{A}$, and $I_C = 1.2\text{ mA}$. Find I_B & I_E . [CO-3] 2

- (c) The d.c. alpha of the transistor in the circuit of fig. 3(c) is 0.96 . The voltage drop across $2\text{ k}\Omega$ is 4 V . Determine the base current. [CO-3] 2

 


Fig. 3(c)

- Q4. (a) Draw a self bias circuit and explain quantitatively why such a circuit is an improvement on the fix bias circuit as far as stability is concerned. [CO-4] 2

- (b) Find the analytical expression for the stabilization factor S for self bias. [CO-4] 2

- (c) In the voltage divider circuit of fig. 4(c), an npn germanium transistor with $\beta = 100$ is used. Calculate the coordinates of the point $Q(V_{CE}, I_C)$. [CO-4] 2

 


Fig. 4(c)

- Q5. (a) Draw a family of common source (CS) drain characteristics of an n-channel JFET and explain the shape of these curves. Indicate ohmic region, saturation region and locus of pinch of region using drain characteristics. [CO-4] **2**
- (b) Explain shorthand method for plotting the transfer curve using Shockley equation. [CO-4] **1**
- (c) Sketch the transfer curve defined by $I_{DSS} = 12\text{V}$ & $V_P = -4\text{V}$. [CO-4] **2**
- (d) Given $I_{DSS} = 8\text{mA}$, $V_{GS} = -1\text{V}$ & $V_P = -4\text{V}$, calculate drain current I_D . [CO-4] **1**
- Q6. (a) Define an exclusive OR gate and draw its symbol and logical block diagram. Also give its truth table. [CO-5] **2**
- (b) List the laws and theorems of the Boolean Algebra. [CO-5] **2**
- (c) Use NAND gates only to construct a logic circuit with output $X = A + B \cdot C$ [CO-5] **1**
- (d) Evaluate the Boolean expression [CO-5] **1/2**
- $$f = \bar{A} \cdot \bar{B} + A \cdot B + \bar{B} + C \text{ for } A = 1, B = 0, C = 1$$
- (e) Evaluate the Boolean expression for [CO-5] **1/2**
- $$f = A \cdot B \cdot \bar{C} + \bar{A} \cdot B + A \cdot \bar{B} \text{ for } A = 1, B = 0 \text{ and } C = 1.$$
- (f) Draw explain the logical diagram of a half – adder using XOR gate & realize it with NAND gates only. [CO-5] **1**

