

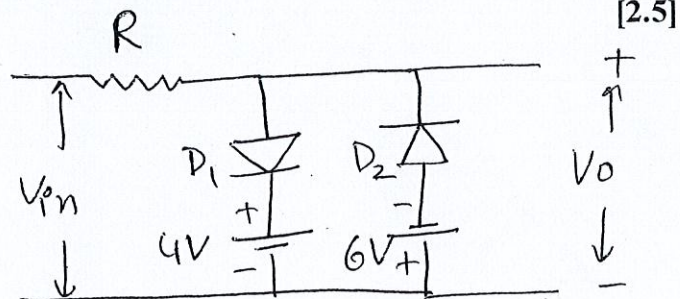
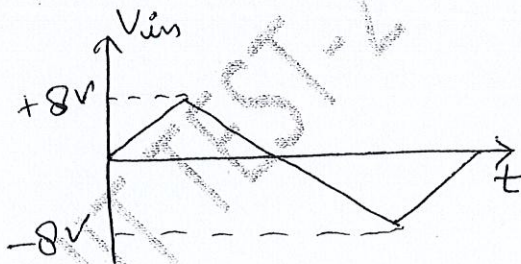


Note: All questions are compulsory. Carrying mobile phone during examinations will be treated as a case of unfair means.

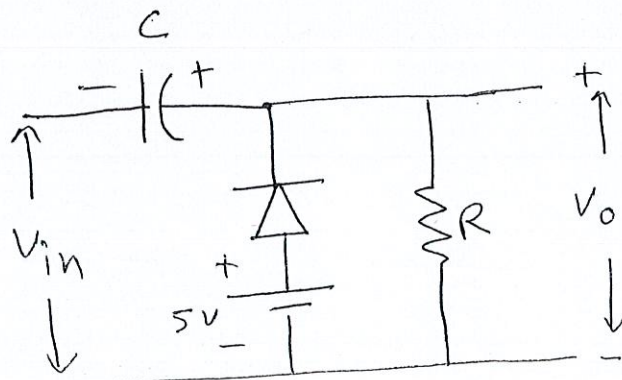- Q1. Derive an expression of ripple factor for full-wave rectifier with resistive load. [3]
- Q2. Compare half-wave, full-wave and bridge rectifier on the basis of efficiency, ripple factor, peak inverse voltage (PIV) and transformer utilization factor (TUF). [2]
- Q3. An a.c. supply of 230 volts is applied to a half-wave rectifier circuit through transformer of turns ratio 5:1. Assume diode as an ideal diode. The load resistance is  $300\Omega$ . Find-
- DC output voltage [2+1+1+1]
  - Peak Inverse Voltage
  - Maximum value of the power delivered to the load
  - Average value of the power delivered to the load
- Q4. Sketch the output waveform with proper explanation for the given clipper circuit. Assume diode is an ideal diode. [2.5]



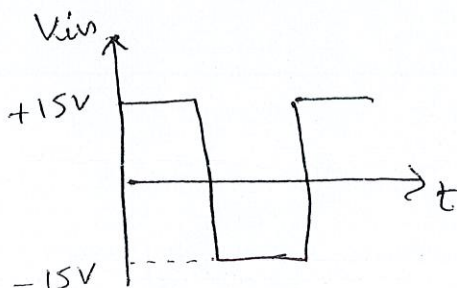- Q5. Explain the working of the given clamper circuit and draw the output waveform. Assume diode as an ideal diode. [2.5]



Q6. Write down the characteristics of ideal op-amp. And derive the expression of closed loop gain for non-inverting amplifier. [2+3]

Q7. Derive the expression of output voltage for following two circuits-

[2.5+2.5]

