

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -3 EXAMINATION- May 2019

B.Tech 2nd Semester

COURSE CODE: 10B11EC211

MAX. MARKS:35

COURSE NAME: Basic Electronic Devices and Circuits

COURSE CREDITS: 4

MAX. TIME: 2 Hrs


Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

Q1. (a) Draw the circuit diagram and output waveform of following clamper circuit-

- (i). Biased positive clamper (ii). Biased negative clamper [4]

In both circuits take square wave of 5volt p-p as input signal and bias voltage of 3 volts.

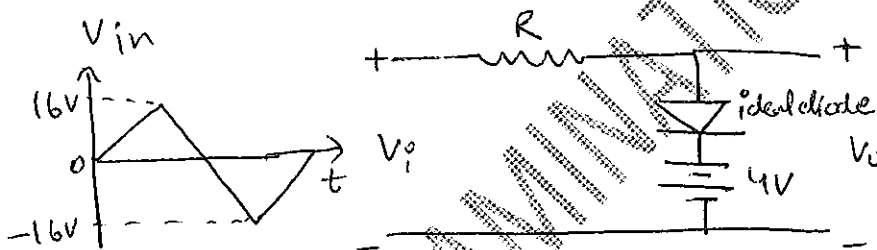
(b) Draw the output wave form for the given circuit with explanation [3]




Q2 (a) Draw the pin diagram of IC 741. Also explain the concept of virtual ground in an op-amp. [3.5]

(b) Define α , β and γ of a transistor and derive the relationship between α and β . [3.5]

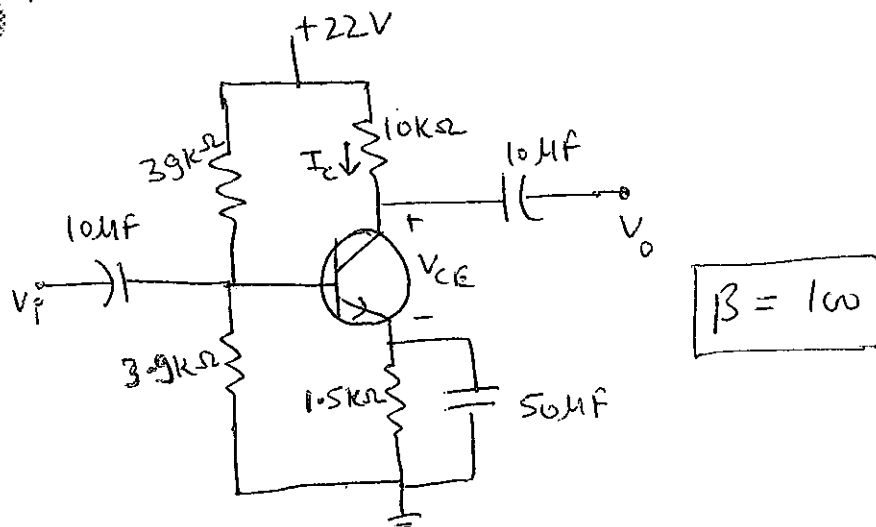Q3 (a). Determine co-ordinates of Q point for the given voltage divider bias circuit: [3.5]



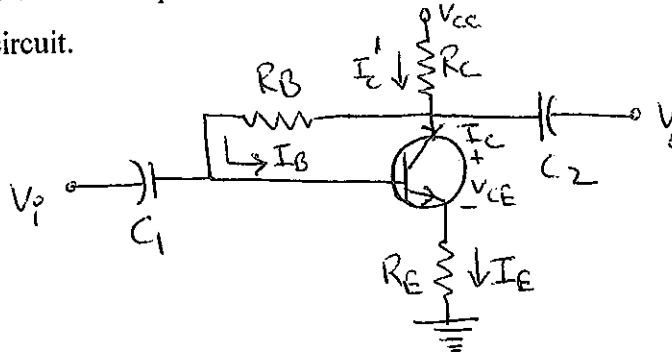- (b). Derive the expression for I_B , I_C and V_{CE} for the given collector feedback bias circuit. [3.5]



- Q4 (a). Explain the construction and working of Junction Field Effect Transistor with neat diagram. [3]
- (b). Draw the drain and transfer characteristics of n-channel JFET and define I_{DSS} , V_{GS} and V_P . [4]
- Q5 (a.) What are the two types of MOSFET? How do they differ in their structure? Briefly explain the working of enhancement type MOSFET with diagram. [5]
- (b). write down the differences between BJT and FET. [2]