
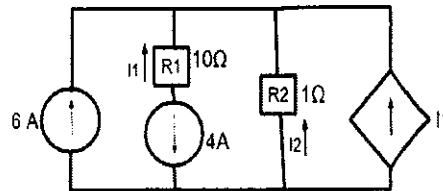


Note: All questions are compulsory. Marks are indicated against each question in square brackets.

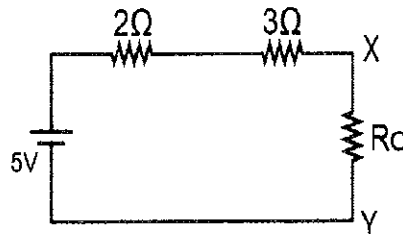
Q1. Write down the statement of Kirchoff's Current Law. For the circuit in the given Figure, compute the current through resistor R3 if it is known that the voltage source supplies a current of 3 A. [5]



Q2. Determine the value of R_o to deliver Maximum power to the resistor, R_o : [5]




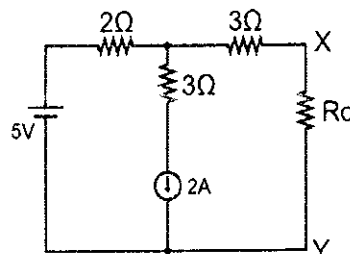Q3. Considering R_o as load resistance, determine the Norton Resistance across terminals X-Y terminals: [5]



Q4. Use voltage division to determine V_x in the given circuit.

[5]

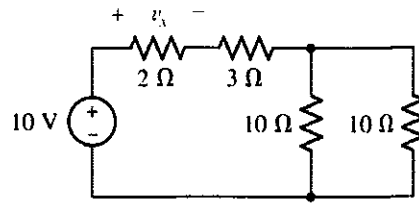

Q5. Write down the statement of the following network theorems-

[5]

- (a). Thevenin's Theorem
- (b). Superposition Theorem.
- (c). Maximum Power Transfer Theorem
- (d). Current Division and Voltage Division
- (e). Reciprocity Theorem