

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT
 TEST -2 EXAMINATIONS-2022

B.Tech-III Semester (ECE)

COURSE CODE (CREDITS): 18B11EC313(4)

MAX. MARKS: 25

COURSE NAME: Electronic Devices and Circuits

COURSE INSTRUCTORS: Er. Munish Sood



MAX. TIME: 1 Hour and 30 Minutes

Note: All questions are compulsory. Marks are indicated against each question in square brackets.

Q1. For the network of Fig.1 calculate

[5] CO-2 , CO-3

- I_B, I_C and r_e
- Z_i and Z_o and A_v

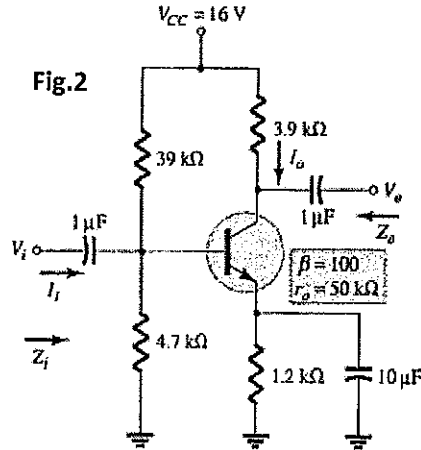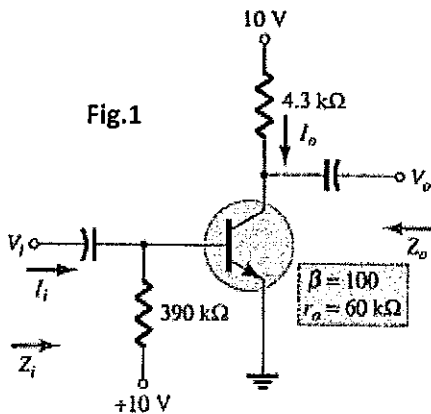

Q2. For the network of Fig.2 calculate

[5] CO-2 , CO-3

- I_E and r_e
- Z_i and Z_o and A_v

Q3) For the network of Fig. 3 calculate

[5] CO-2 , CO-3

- Z_i, Z_o
- A_v and V_o if $V_i = 1$ mV

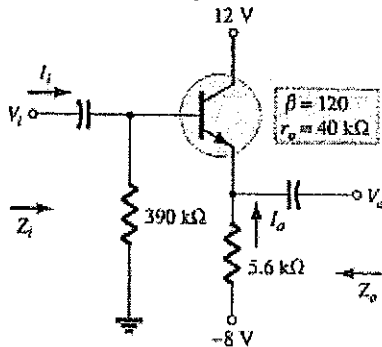


Fig.3

Q4) Determine V_o for the network of Fig.4

[3] CO-1

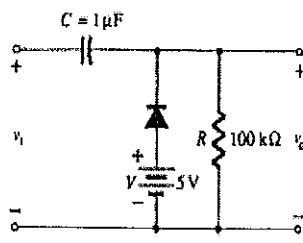
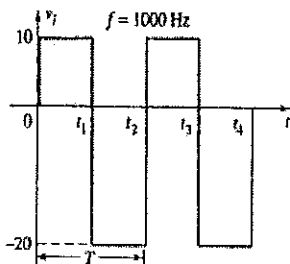


Fig.4

Q5) In the CASCODE amplifier of Fig.5

[7] CO-2 & CO-3

- Calculate the DC bias voltage V_{B1} , V_{B2} and V_{C2} .
- Calculate the Voltage Gain A_V and output voltage V_O .

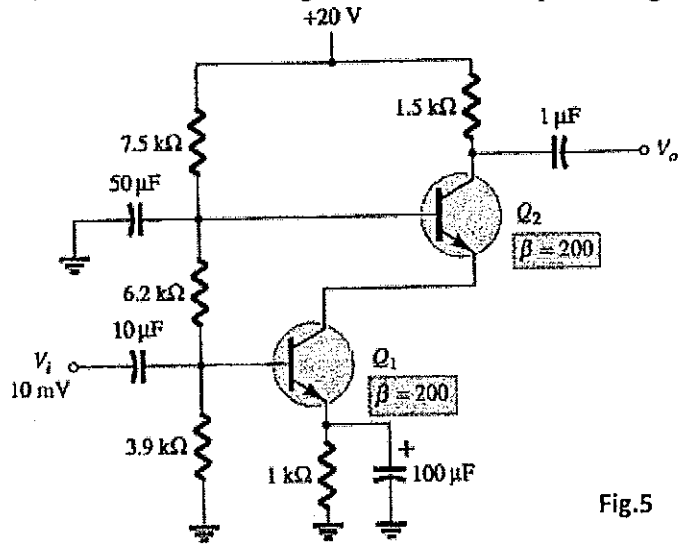


Fig.5