

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT
T2 EXAMINATIONS, OCTOBER-2019

B.Tech Vth Semester (ECE)

Course Code: 17B11EC513


MAX. MARKS: 25

Course Name: Course Credits: 04

MAX. TIME: 1.5 Hour

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means. Marks are indicated in square brackets against each question.

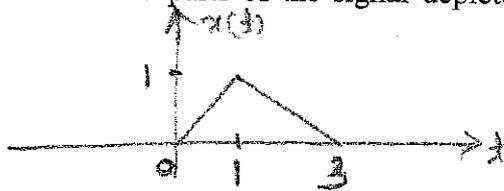- Q1. (a)** Sketch the even and odd parts of the signal depicted in figure. Label and sketch carefully. [2] [CO1, CO2]



- (b)** Find the initial and final values, if they exist, of the signals with LT given below

(i) $F(s) = \frac{s+10}{s^2+3s+2}$

(ii) $F(s) = \frac{s^2+5s+7}{s^2+3s+2}$ [2]

- (c)** Write the *h*-parameters of the network in terms of *z*-parameters. [1]

- Q2. (a)** Write the properties of Hurwitz polynomial. [2] [CO1, CO4]
- (b)** Test the following polynomials for the Hurwitz property: [3]

(i) $P(s) = s^3 + 2s^2 + s + 2$

(ii) $P(s) = s^4 + 3s^2 + 4$

- Q3. (a)** Define Positive Real Function (PRF). [1] [CO1, CO4]
- (b)** Determine whether the following functions are PRF [4]

(i) $F(s) = \frac{s+3}{s^2+5s+1}$

(ii) $F(s) = \frac{5s^2+s}{s^2+1}$

- Q4. (a)** Write the properties of RL impedance or RC admittance. [2] [CO1, CO4]
- (b)** Synthesize the given network function in Cauer-I form. [3]

$$F(s) = \frac{(s+4)(s+6)}{(s+3)(s+5)}$$

- Q5. (a)** Synthesize the LC-driving point impedance [2.5] [CO1, CO4]

$$Z(s) = \frac{6s^4 + 42s^2 + 48}{s^5 + 18s^2 + 48s}$$

in Foster-II form.

- (b)** For given pole-zero diagram, that represents an RL impedance, synthesize in a series Foster form. [2.5]

