

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT  
 TEST -3 EXAMINATION-2022  
 B.Tech-III Semester (ECE/ECM)



COURSE CODE (CREDITS): 18B11EC313(4)  
 COURSE NAME: Electronic Devices and Circuits  
 COURSE INSTRUCTORS: Er. Munish Sood

MAX. MARKS: 35

MAX. TIME: 2 Hours


Note: All questions are compulsory. Marks are indicated against each question in square brackets.

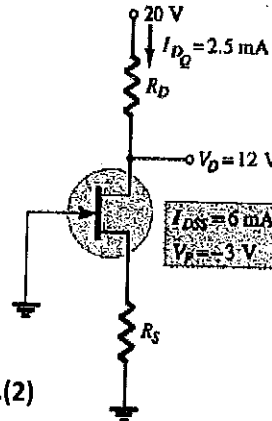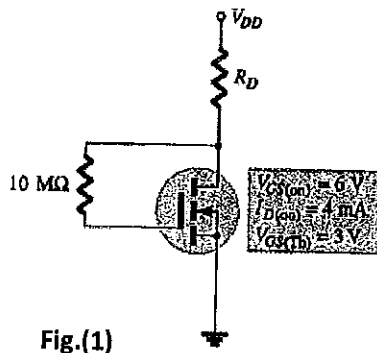Q1. The levels of  $V_{DS}$  and  $I_D$  are specified as  $V_{DS} = 1/2 V_{DD}$  and  $I_D = I_{D(on)}$  for the network of following Fig.(1). Determine the levels of  $V_{DD}$  and  $R_D$ . [ 5] CO4



Q2) For the network of Fig.(2) the levels of  $V_D$  and  $I_{DQ}$  are specified. Determine the required values of  $R_D$  and  $R_S$ . [5] CO4

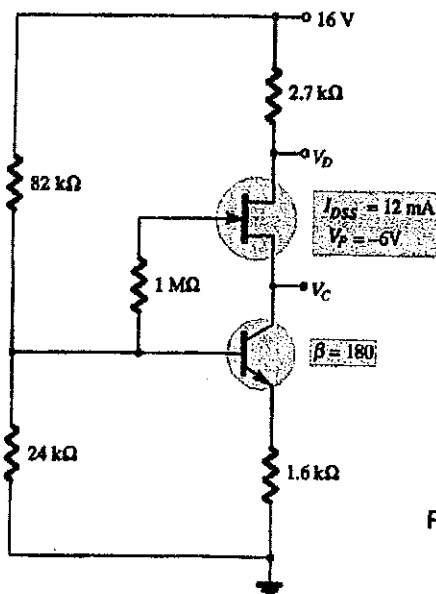Q3) Determine the level of  $V_D$  and  $V_C$  for the network of Fig.(3). [5] CO2&CO3



Q4) For the network of Fig.(4) determine  $V_{GSQ}$ ,  $I_{DQ}$ ,  $Z_i$ ,  $Z_o$  and  $A_v$ .

[5] CO5

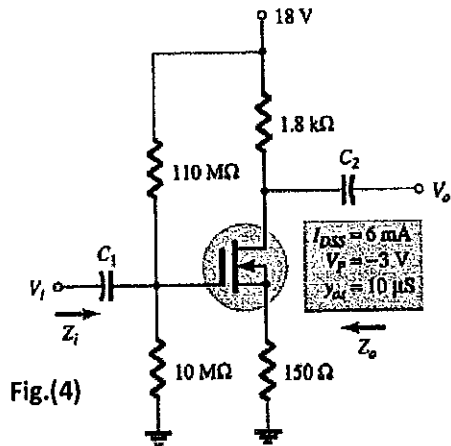


Fig.(4)

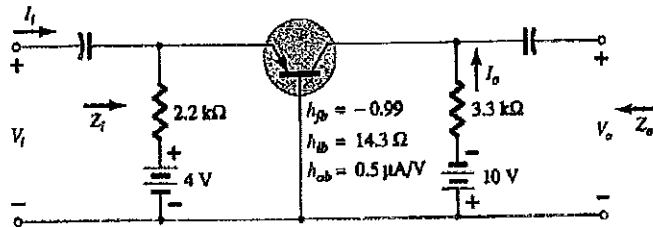


Fig.(5)

Q5) For the network of Fig.(5), determine  $Z_i$ ,  $Z_o$ ,  $A_v$  and  $A_i$ . [5]CO3

Q6) For the cascade amplifier of network of Fig.(5) calculate dc bias, input impedance, output impedance, voltage gain and output voltage. [5]CO6

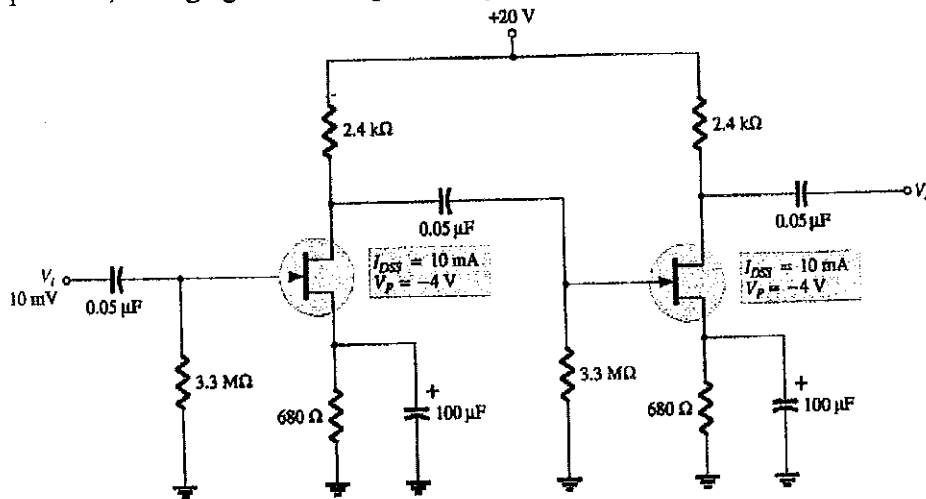


Fig.(6)

Q7) Determine for the network of Fig.(7) [5]CO1

- (i)  $V_L, I_L, I_Z$  and  $I_R$  for the following network with  $R_L = 470$  ohms.
- (ii) The minimum value of  $R_L$  to ensure that the Zener diode is in the on state.

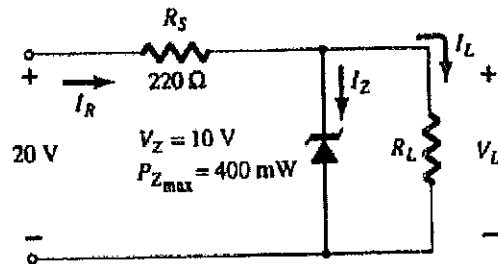


Fig.(7)