

Pradeep Crang

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY WAKNAGHAT

MID-SEM EXAMINATION (SUMMER SEM. JUNE 2018)

B.Tech 4<sup>th</sup> Sem. (ECE)

COURSE CODE: 10B11EC401

MAX. MARKS: 50

COURSE NAME: Digital Electronics

COURSE CREDITS: 4

MAX. TIME: 2-Hrs.

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

- Q1. Convert  $(8FD)_{16}$  into gray and 9's complement formats. (2.5+2.5=5)
- Q2(a). Subtract 27.50 from 68.75 using the 12 bit 1's complement arithmetic. (3)
- Q2(b). Given that  $16_{10} = 100_b$ , find the value of b. (1)
- Q2(c). What do you mean by a position-weighted system? (1)
- Q3(a). Given the 8-bit data word 10111001, generate the 12-bit composite word for the Hamming code.
- Q3(b). Introduce a 1-bit error in the code word obtained in part a at 11<sup>th</sup> position, now show the steps to detect and correct this error. Show the error vector and corrected code-word. (3.5+3.5=7)
- Q4. Find the values of the two-valued variables A, B, C, and D by solving the set of simultaneous equations:
- $$\bar{A} + AB = 0, \quad AB = AC, \quad AB + A\bar{C} + CD = \bar{C}D \quad (5)$$
- Q5. Show that  $AB + A\bar{B}C + B\bar{C} = AC + B\bar{C}$  (3)
- Q6. Reduce the following expression using K-map and implement the reduced expression using universal gate and AOI logic.  
 $F = M(1, 4, 5, 11, 12, 14). d(6, 7, 15)$  (5)
- Q7. Reduce the following expression using K-map and implement the reduced expression using universal gate.  
 $F = A\bar{B}C + B + B\bar{D} + AB\bar{D} + \bar{A}C$  (5)

- Q8. Design a BCD to gray code converter. (5)
- Q9. Design a 4-bit binary parallel adder-subtractor (in one circuit). (5)
- Q10. Design a parity generator to generate even parity for 3 bit word using 4:1 MUX. (5)

JUIT MID-SEM EXAM. (SUMMER SEM JUNE 2018)