

JAYPEE UNIVERSITY OF INFORMATION TECHNOLOGY, WAKNAGHAT

TEST -1 EXAMINATION- February 2018

B.Tech 4th Semester

COURSE CODE:10B11EC401

MAX. MARKS: 15

COURSE NAME: Digital Electronics

COURSE CREDITS: 4

MAX. TIME: One Hr

Note: All questions are compulsory. Carrying of mobile phone during examinations will be treated as case of unfair means.

1. Match List-I with List-II and select the correct answer using the codes given below the lists. [2 Marks]


List - I

- a. $A \oplus B = 0$
- b. $\overline{A+B} = 0$
- c. $\overline{A} \cdot B = 0$
- d. $A \oplus B = 1$

List - II

- 1. $A \neq B$
- 2. $A = B$
- 3. $A = 1$ or $B = 1$
- 4. $A = 1$ or $B = 0$

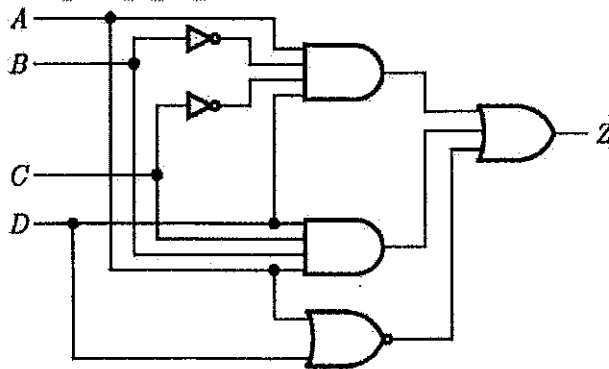
2. In the following circuit find the simplified output Z in terms of A, B, C and D. [2 Marks]




3. Find the minimum number of NAND gates required to implement the Boolean function $A + AB + \overline{A}BC$ [1Marks]

4. Draw a logic circuit with inputs A, B and C that control the passage of a signal according to the following requirements: [2 Marks]
- a. Output X will equal A when control input B and C are the same.
 - b. X will remain HIGH when B and C are different.

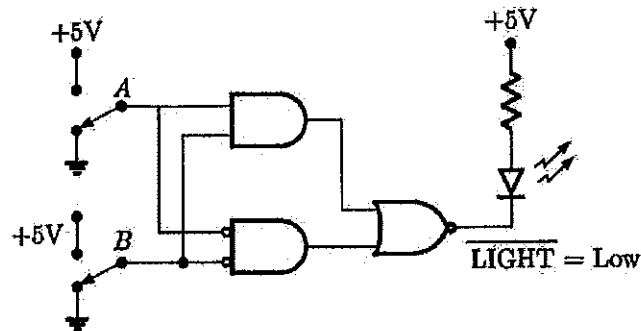5. Consider the given circuit diagram of switching of light from two different switches. What are the input values of switches so as to turn on the LED? [2 Marks]



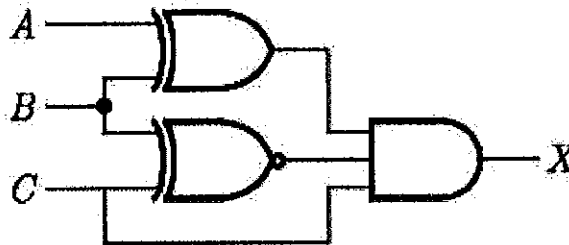6. In circuit shown below, for what input at the terminals A, B and C the output is $X = 1$? [1 Marks]



7. Perform the following arithmetic operations with hexadecimal numbers: [2 Marks]

(i) $2BFC + 54A7$

(ii) $AC74 - B3F$

8. Reduce the following expression to the simplest possible POS and SOP forms: [3 Marks]

$$f = \sum m(6,9,13,18,19,25,27,29,31) + d(2,3,11,15,17,24,28)$$