

Also available as



Revised **1st** Edition

BASIC ELECTRICAL ENGINEERING



D C KULSHRESHTHA

Mc
Graw
Hill
Education





Basic Electrical Engineering

(Revised First Edition)

D C KULSHRESHTHA

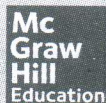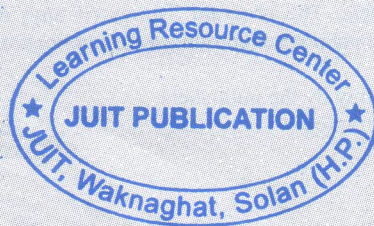*Professor of Electronics and Communication Engineering
Jaypee University of Information Technology
Waknaghat, Distt. Solan (Himachal Pradesh)*



McGraw Hill Education (India) Private Limited

NEW DELHI

McGraw Hill Education Offices

New Delhi New York St Louis San Francisco Auckland Bogotá Caracas
Kuala Lumpur Lisbon London Madrid Mexico City Milan Montreal
San Juan Santiago Singapore Sydney Tokyo Toronto



McGraw Hill Education (India) Private Limited

Published by McGraw Hill Education (India) Private Limited
P-24, Green Park Extension, New Delhi 110 016

Basic Electrical Engineering (Revised First Edition)

Copyright © 2012, 2009 by McGraw Hill Education (India) Private Limited

Twelfth reprint 2016
RBCBCRAQDRLRX

No part of this publication may be reproduced or distributed in any form or by any means, electronic, mechanical, photocopying, recording, or otherwise or stored in a database or retrieval system without the prior written permission of the publishers. The program listings (if any) may be entered, stored and executed in a computer system, but they may not be reproduced for publication.

This edition can be exported from India only by the publishers,
McGraw-Hill Education (India) Private Limited

ISBN (13 digits): 978-0-07-132896-8

ISBN (10 digits): 0-07-132896-3

Managing Director: *Kaushik Bellani*

Head—Higher Education Publishing and Marketing: *Vibha Mahajan*

Publishing Manager (SEM & Tech Ed.): *Shalini Jha*

Manager—Production Systems: *Satinder S Baveja*

Asst. Manager—Production: *Anjali Razdan*

General Manager—Production: *Rajender P Ghansela*

Information contained in this work has been obtained by McGraw Hill Education, from sources believed to be reliable. However, neither McGraw Hill Education nor its authors guarantee the accuracy or completeness of any information published herein, and neither McGraw Hill Education nor its authors shall be responsible for any errors, omissions, or damages arising out of use of this information. This work is published with the understanding that McGraw Hill Education and its authors are supplying information but are not attempting to render engineering or other professional services. If such services are required, the assistance of an appropriate professional should be sought.

Typeset at Tej Composers, WZ 391, Madipur Village, New Delhi 110 063, and text and cover printed at A.P. Offset Pvt. Ltd., 25/487, Zulf-e-Bengal, Dilshad Garden, New Delhi 110 095

Visit us at: www.mheducation.co.in

CONTENTS

<i>About the Author</i>	ii
<i>Foreword</i>	vi
<i>Preface</i>	vii
<i>Walkthrough</i>	xviii
<i>Scientific Calculator</i>	xxi
<i>Standard Symbols</i>	xxii
<i>Notations</i>	xxiii
1. INTRODUCTION	1
1.1 Charge	1
1.2 Voltage or Potential	4
1.3 Basic Circuit	6
1.4 Units and Symbols	7
<i>Rules to Use SI Prefixes</i>	8
<i>Guidelines for Using SI Units</i>	8
1.5 Basics of Experimentation	10
<i>General Instructions and Precautions</i>	10
2. OHM'S LAW	14
2.1 Ohm's Law	14
2.2 Resistance	15
2.3 Duality	28
2.4 Conductors and Resistors	28
2.5 Variation of Resistance with Temperature	30
<i>Additional Solved Examples</i>	32
<i>Summary</i>	39
<i>Check Your Understanding</i>	40
<i>Review Questions</i>	41
<i>Multiple Choice Questions</i>	41
<i>Problems</i>	42
<i>Experimental Exercise</i>	47
3. NETWORK ANALYSIS	50
3.1 Network Components	50
3.2 Series and Parallel Combinations	54
3.3 Energy Sources	57
3.4 Combination of Sources	62
3.5 Types of Sources	66
3.6 Kirchhoff's Laws	67
3.7 Loop-Current Analysis	72
3.8 Mesh Analysis	75

3.9	Node-Voltage Analysis	80
3.10	Nodal Analysis	84
3.11	Choice of Method of Analysis	85
	<i>Additional Solved Examples</i>	85
	<i>Summary</i>	93
	<i>Check Your Understanding</i>	94
	<i>Review Questions</i>	95
	<i>Multiple Choice Questions</i>	95
	<i>Problems</i>	96
	<i>Experimental Exercises</i>	100
4.	NETWORK THEOREMS	
4.1	Introduction	104
4.2	Superposition Theorem	104
4.3	Thevenin's Theorem	108
4.4	Norton's Theorem	112
4.5	Maximum Power Transfer Theorem	113
4.6	Millman's Theorem	116
4.7	Reciprocity Theorem	116
4.8	Tellegen's Theorem	117
	<i>Additional Solved Examples</i>	119
	<i>Summary</i>	128
	<i>Check Your Understanding</i>	129
	<i>Review Questions</i>	130
	<i>Multiple Choice Questions</i>	130
	<i>Problems</i>	131
	<i>Experimental Exercises</i>	134
5.	ELECTROMAGNETISM	
5.1	Introduction	141
5.2	Magnetic Field due to Electric Current	141
5.3	Force on Current-Carrying Conductor	144
5.4	Torque Experienced by a Coil	146
5.5	Force between Parallel Conductors	147
5.6	Electromagnetic Induction	148
5.7	Methods of Producing Induced EMF	150
5.8	Dynamically Induced EMF	150
5.9	Electromagnetic Induction and Lorentz Force	153
	<i>Additional Solved Examples</i>	156
	<i>Summary</i>	159
	<i>Check Your Understanding</i>	160
	<i>Review Questions</i>	161
	<i>Multiple Choice Questions</i>	161
	<i>Problems</i>	163
6.	MAGNETIC CIRCUITS	
6.1	Introduction	164
6.2	Magnetomotive Force (MMF)	164
6.3	Magnetic Circuit Theory	166
	<i>Additional Solved Examples</i>	173
	<i>Summary</i>	178
	<i>Check Your Understanding</i>	179

Review Questions 180
 Multiple Choice Questions 180
 Problems 180

7. SELF- AND MUTUAL INDUCTANCES

183

- 7.1 Self-Inductance 183
- 7.2 Inductors 186
- 7.3 Mutual Inductance 186
- 7.4 Dot Convention 189
- 7.5 Coupled Coils in Series 191
- 7.6 Coupled Coils in Parallel 193
- 7.7 Energy Stored in Magnetic Field 195
- 7.8 Lifting Power of a Magnet 196
- Additional Solved Examples 196
- Summary 199
- Check Your Understanding 200
- Review Questions 201
- Multiple Choice Questions 201
- Problems 202

8. DC TRANSIENTS

204

- 8.1 Introduction 204
- 8.2 The Simple *RL* Circuit 205
- 8.3 The Simple *RC* Circuit 212
- 8.4 DC-Excited Single-Capacitor *RC* and Single-Inductor *RL* Circuits 216
- 8.5 *RC* Timers 219
- Additional Solved Examples 220
- Summary 228
- Check Your Understanding 229
- Review Questions 229
- Multiple Choice Questions 230
- Problems 231

9. ALTERNATING VOLTAGE AND CURRENT

233

- 9.1 Introduction 233
- 9.2 Sinusoidal Functions—Terminology 234
- 9.3 Concept of Phasors 242
- 9.4 Algebraic Operations on Phasors 244
- 9.5 Mathematics of Complex Numbers 246
- 9.6 Power and Power Factor 254
- 9.7 Behaviour of *R*, *L* and *C* in *AC* Circuits 256
- Additional Solved Examples 262
- Summary 266
- Check Your Understanding 268
- Review Questions 268
- Multiple Choice Questions 269
- Problems 269

10. AC CIRCUITS

272

- 10.1 Series *RL* Circuit 272
- 10.2 Series *RC* Circuit 275
- 10.3 Complex Power 276
- 10.4 Parallel *RL* Circuit 278

10.5	Parallel RC Circuit	278
10.6	Series RLC Circuit	280
10.7	Parallel RLC Circuit	282
10.8	Network Theorems Applied to AC Circuits	283
	<i>Additional Solved Examples</i>	286
	<i>Summary</i>	294
	<i>Check Your Understanding</i>	295
	<i>Review Questions</i>	296
	<i>Multiple Choice Questions</i>	297
	<i>Problems</i>	298
	<i>Experimental Exercises</i>	300
11.	RESONANCE IN AC CIRCUITS	
11.1	Introduction	310
11.2	Series Resonant Circuit	310
11.3	Different Aspects of Resonance	312
11.4	Resonance Curve	318
11.5	Parallel Resonant Circuit	320
11.6	Comparison between Series and Parallel Resonance	324
	<i>Additional Solved Examples</i>	326
	<i>Summary</i>	329
	<i>Check Your Understanding</i>	331
	<i>Review Questions</i>	331
	<i>Multiple Choice Questions</i>	332
	<i>Problems</i>	333
12.	THREE-PHASE CIRCUITS AND SYSTEMS	
12.1	Introduction	335
12.2	Double-Subscript Notation	336
12.3	Concept of Three-Phase Voltages	337
12.4	Generation of Three-Phase Voltages	338
12.5	Three-Phase Loads	339
12.6	Star (Y)-Connected Three-Phase System	340
12.7	Delta (Δ)-Connected Three-Phase System	342
12.8	Voltages and Currents Relations in 3- ϕ Systems	343
12.9	Power in Three-Phase System with a Balanced Load	350
12.10	Comparison between Two Three-Phase Systems	351
12.11	Measurement of Power	352
	<i>Additional Solved Examples</i>	356
	<i>Summary</i>	364
	<i>Check Your Understanding</i>	365
	<i>Review Questions</i>	365
	<i>Multiple Choice Questions</i>	366
	<i>Problems</i>	367
	<i>Experimental Exercise</i>	369
13.	TRANSFORMERS	
13.1	Introduction	372
13.2	Principle of Operation	373
13.3	Ideal Transformer	374
13.4	Practical Transformer at No Load	379
13.5	Construction of Transformer	383

310

335

372

- 13.6 Transformer on Load 384
- 13.7 Practical Transformer on Load 386
- 13.8 Equivalent Circuit of a Transformer 387
- 13.9 Voltage Regulation of a Transformer 390
- 13.10 Efficiency of a Transformer 394
- 13.11 Autotransformers 397
- 13.12 Three-Phase Transformers 400
- 13.13 Some Special Transformers 401
- 13.14 Transformer Testing 402
 - Additional Solved Examples* 404
 - Summary* 410
 - Check Your Understanding* 411
 - Review Questions* 412
 - Multiple Choice Questions* 412
 - Problems* 414
 - Experimental Exercises* 417

14. ALTERNATORS AND SYNCHRONOUS MOTORS

425

- 14.1 Electromechanical Energy-Conversion Machines 425
- 14.2 Synchronous Machines 431
- 14.3 Construction of Alternators 433
- 14.4 Rotating Magnetic Flux Due to Three-Phase Currents 436
- 14.5 Armature Winding 438
- 14.6 EMF Equation 440
- 14.7 Armature Reaction 442
- 14.8 Equivalent Circuit of an Alternator 444
- 14.9 Power Delivered by an Alternator 448
- 14.10 Measurement of Synchronous Impedance 449
- 14.11 Synchronous Motors 451
- 14.12 Power Developed by a Synchronous Motor 454
- 14.13 Operation of a Synchronous Motor 456
- 14.14 Synchronous Condenser 458
 - Additional Solved Examples* 459
 - Summary* 469
 - Check Your Understanding* 470
 - Review Questions* 471
 - Multiple Choice Questions* 472
 - Problems* 474

15. INDUCTION MOTORS

476

- 15.1 Introduction 476
- 15.2 Principle of Working 476
- 15.3 Construction of Induction Motor 479
- 15.4 Rotor EMF, Current and Power Factor 481
- 15.5 Power Relations for an Induction Motor 484
- 15.6 Equivalent Circuit of an Induction Motor 486
- 15.7 Torque-Slip Characteristics 491
- 15.8 Starting of Induction Motors 496
 - Additional Solved Examples* 498
 - Summary* 502
 - Check Your Understanding* 503

- Review Questions* 504
- Multiple Choice Questions* 505
- Problems* 506
- Experimental Exercise* 508

16. DC MACHINES

- 16.1 Importance 513
- 16.2 Construction of a DC Machine 514
- 16.3 Armature Current and Flux 516
- 16.4 Armature Winding 516
- 16.5 EMF Equation for a DC Generator 519
- 16.6 Types of DC Machines 520
- 16.7 Armature Reaction 526
- 16.8 Losses in a DC Machine 527
- 16.9 Efficiency of a DC Generator 528
- 16.10 Characteristics of DC Generators 529
- 16.11 DC Motors 535
- 16.12 Torque Developed by a DC Motor 537
- 16.13 Torque and Speed Characteristics of a DC Motor 538
- 16.14 Starting of DC Motors 542
 - Additional Solved Examples* 543
 - Summary* 549
 - Check Your Understanding* 550
 - Review Questions* 551
 - Multiple Choice Questions* 551
 - Problems* 553
 - Experimental Exercises* 555

17. FRACTIONAL HORSEPOWER MOTORS

- 17.1 Introduction 561
- 17.2 Problem with Single-Phase Motor 562
- 17.3 Types of Single-Phase Motors 566
- 17.4 AC Series Motor 571
- 17.5 Universal Motor 572
- 17.6 Geneva Cam 573
- 17.7 Stepper Motors 573
- 17.8 Variable Reactance (VR) Stepper Motors 574
- 17.9 Permanent Magnet (PM) Stepper Motors 579
- 17.10 Hybrid Stepper Motors 582
 - Summary* 584
 - Check Your Understanding* 585
 - Review Questions* 585
 - Multiple Choice Questions* 586
 - Problems* 588

18. ELECTRICAL MEASURING INSTRUMENTS

- 18.1 Classification of Instruments 589
- 18.2 Principle of Operation 590
- 18.3 Essentials of an Instrument 591
- 18.4 Moving Coil Instruments 596
- 18.5 Permanent Magnet Moving Coil (PMMC) Instruments 596
- 18.6 Dynamometer-Type Instruments 599

18.7	Moving-Iron Instruments	600	
18.8	Ammeters and Voltmeters	602	
18.9	Resistance Measurement	610	
18.10	Meter Sensitivity (Ohms-per-volt Rating)	612	
18.11	Multimeter	613	
18.12	Measurement of Power	613	
18.13	Measurement of Energy	616	
	<i>Additional Solved Examples</i>	617	
	<i>Summary</i>	619	
	<i>Check Your Understanding</i>	620	
	<i>Review Questions</i>	621	
	<i>Multiple Choice Questions</i>	622	
	<i>Problems</i>	623	
19.	ELECTRICAL INSTALLATION AND ILLUMINATION		624
19.1	Introduction	624	
19.2	Distribution of Electrical Energy	625	
19.3	Wires and Cables for Internal Wiring	626	
19.4	Switches and Circuits	627	
19.5	Electric Wiring Systems	631	
19.6	Types of Wiring	631	
19.7	Other Accessories	634	
19.8	A Typical Control Circuit	636	
19.9	Earthing of Installation	637	
19.10	Safety Precautions in Handling Electrical Appliances	638	
19.11	Testing of Electrical Installation	639	
19.12	Incandescent or Filament Lamp	641	
19.13	Fluorescent Tube	643	
19.14	Compact Fluorescent Lamp (CFL)	644	
19.15	Mercury Vapour Lamp	645	
19.16	Sodium Vapour Lamp	646	
19.17	Neon Lamp	647	
	<i>Summary</i>	648	
	<i>Check Your Understanding</i>	648	
	<i>Review Questions</i>	649	
A	<i>Supplementary Exercises</i>		651
B	<i>Supplementary Exercises</i>		695
C	<i>Supplementary Exercises</i>		719
D	<i>Supplementary Exercises</i>		769
E	<i>Supplementary Exercises</i>		813
	<i>Glossary</i>		829
	<i>Index</i>		845